 


Digital IC Design and Architecture




Combinational Logic and Circuits

Static CMOS Circuit

At every point in time (except during the switching transients) each **gate output is connected to either V_{DD} or V_{ss}** via a low-resistive path.


The outputs of the gates **assume at all times the value of the Boolean function**, implemented by the circuit (ignoring, once again, the transient effects during switching periods).

 This is in contrast to the **dynamic** circuit class, which relies on temporary storage of signal values on the capacitance of high impedance circuit nodes.




V_{out} is Boolean
function of inputs,
 $V_1, V_2, V_3, \dots, V_N$.

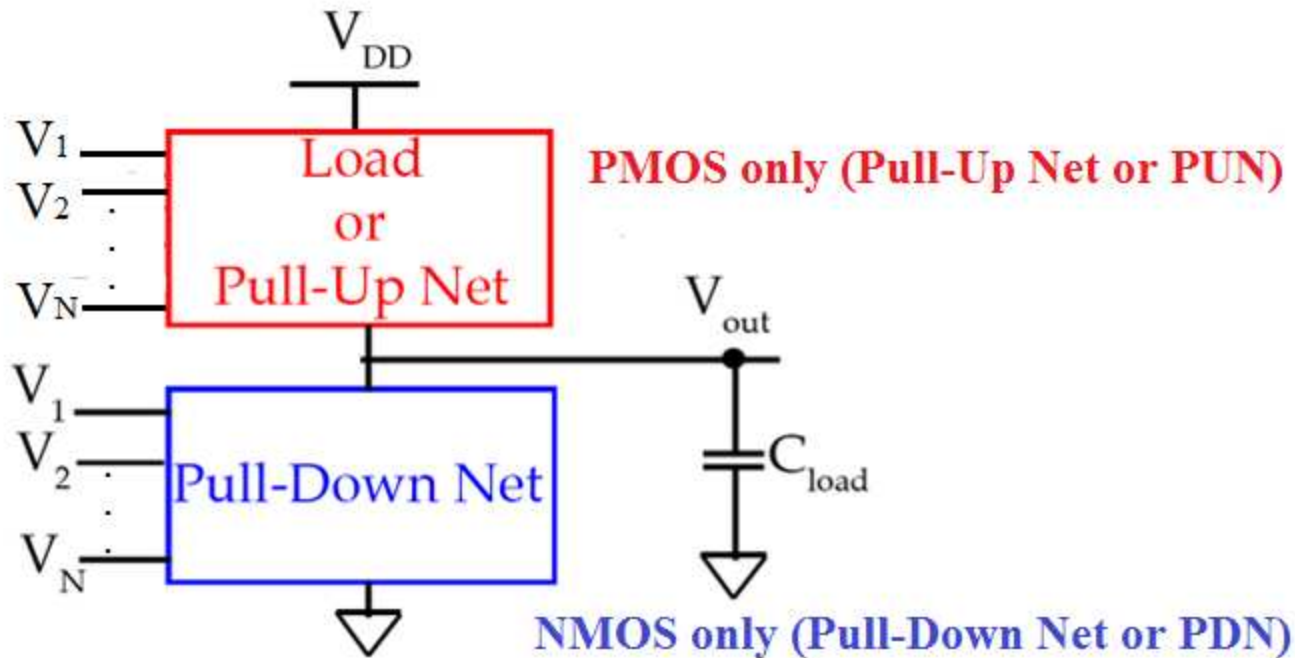"1" $\Rightarrow V_{DD}$
"0" $\Rightarrow 0$



Static Complementary CMOS

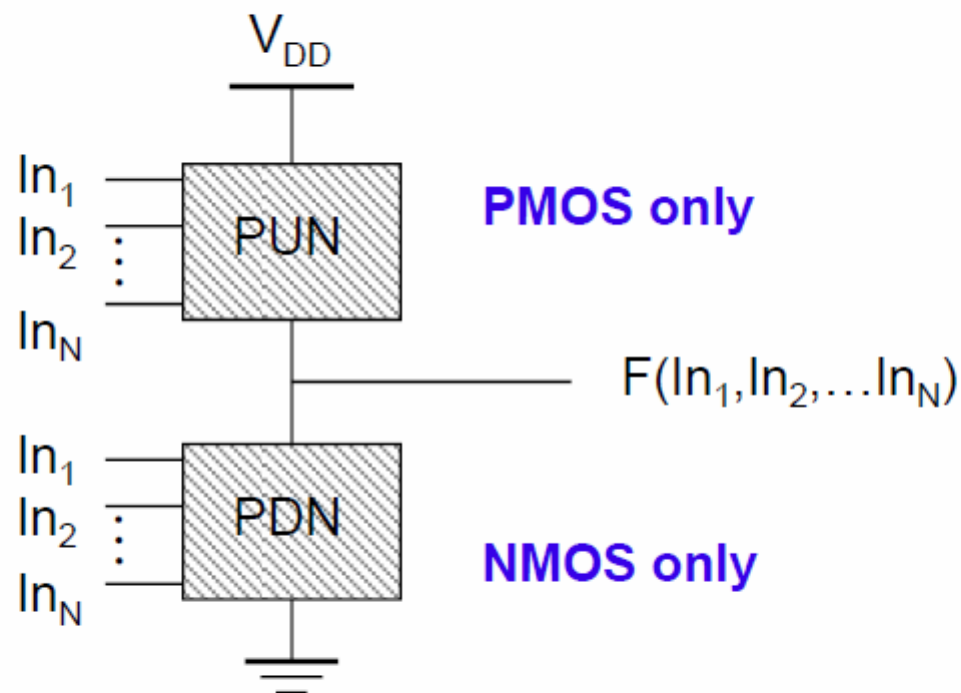


- ♦ PUN and PDN are **dual** logic networks
- ♦ PUN and PDN functions are **complementary**

NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal

 NMOS switch closes when switch control input is high





NMOS Transistors pass a “strong” 0 but a “weak” 1

PMOS Transistors

in Series/Parallel Connection

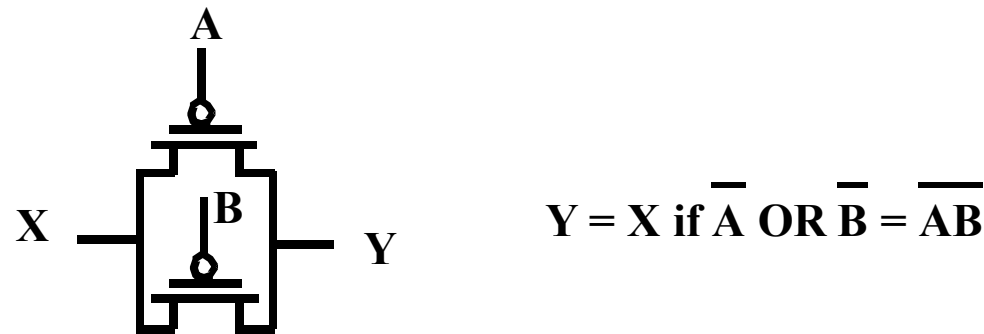
 
PMOS switch closes when switch control input is low





PMOS Transistors pass a “strong” 1 but a “weak” 0

Threshold Drops

PUN – Pull Up Network

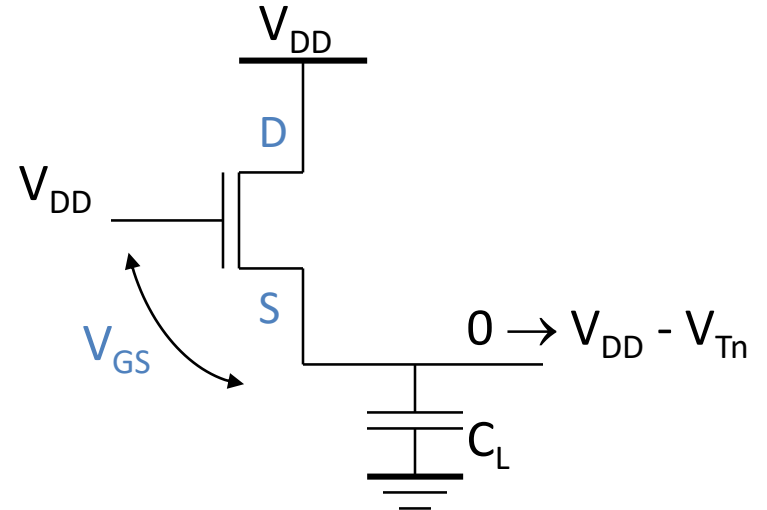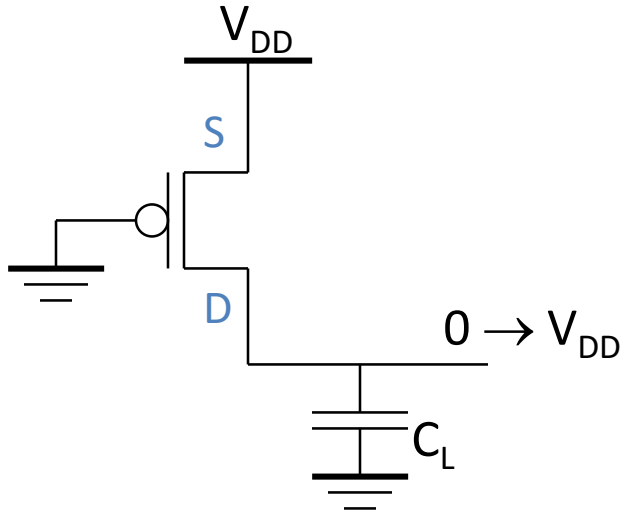

PDN – Pull Down Network

 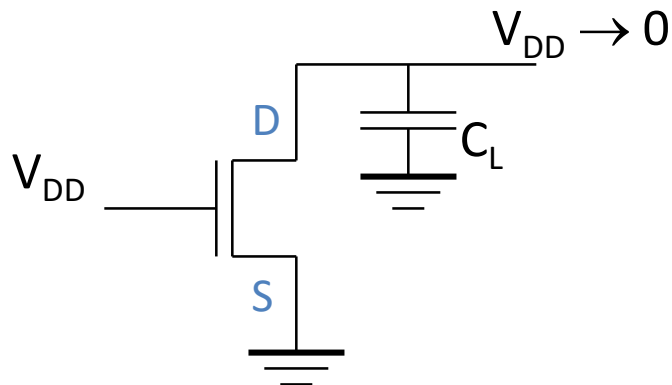


Complementary CMOS Logic Style

- PUP is the DUAL of PDN
(can be shown using DeMorgan's Theorem's)

$$\overline{A + B} = \bar{A}\bar{B}$$

$$\overline{\bar{A}\bar{B}} = A + B$$

- The complementary gate is inverting

 


$$\text{AND} = \text{NAND} + \text{INV}$$

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 

PDN: $G = A B \Rightarrow$ Conduction to GND


PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}

$$G(In_1, In_2, In_3, \dots) \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 

Complex CMOS Gate

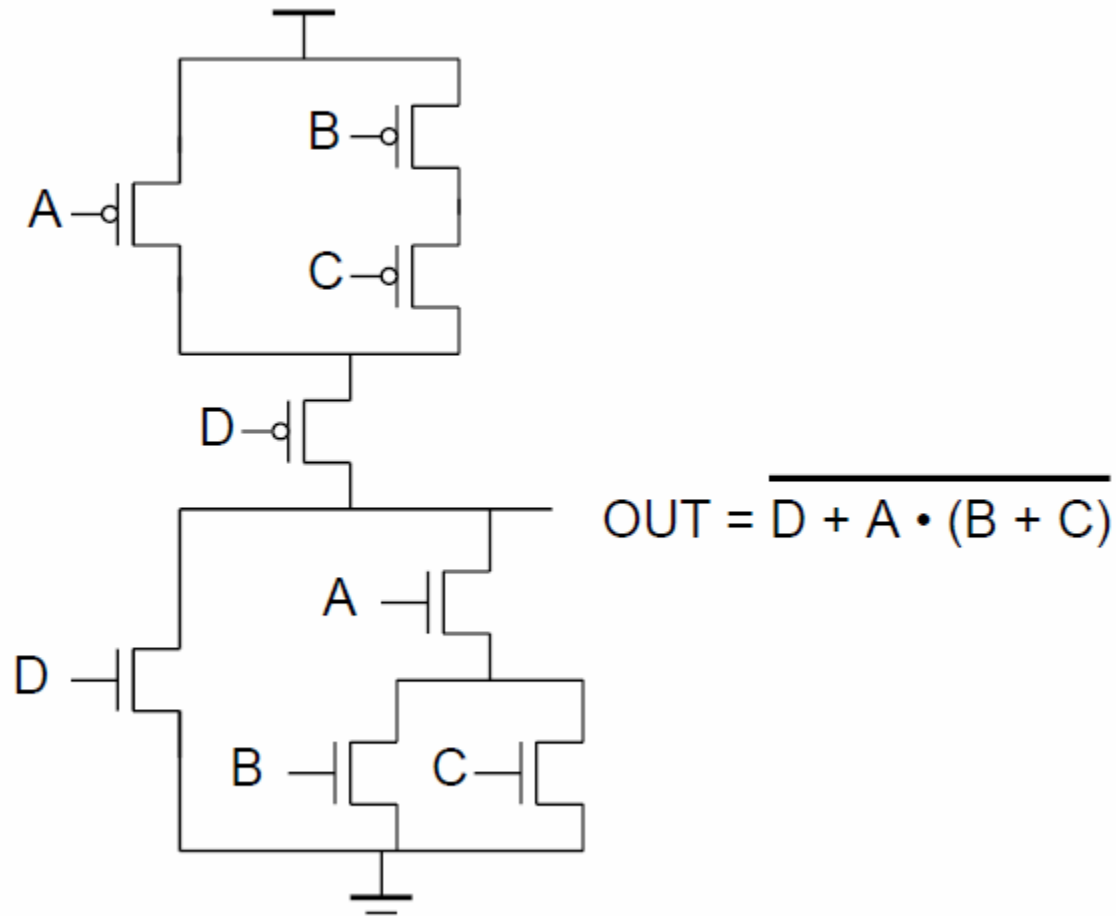

Digital IC Design and Architecture


 


Combinational Logic: CMOS Implementation

CMOS LOGIC GATES


19

2-INPUT NOR (NR2)

  

nMOS Net ON, pMOS Net OFF
or
nMOS Net OFF, pMOS Net ON

CMOS NR2

 

$$V_{th}(NR2) = \frac{V_{Tn} + \frac{1}{2} \sqrt{\frac{k_p}{k_n}} (V_{DD} + V_{Tp})}{1 + \frac{1}{2} \sqrt{\frac{k_p}{k_n}}}$$

$$V_{th}(INV) = \frac{V_{Tn} + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}} (V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}}$$


Symmetrical EQUIV INV

$k_{pEQV} = k_{nEQV}$ or $k_{pEQV}/k_{nEQV} = 1$ and $V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(INV) = V_{DD}/2$

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$

PARASITIC CAPS FOR CMOS NR2 (CONSERVATIVE)

22

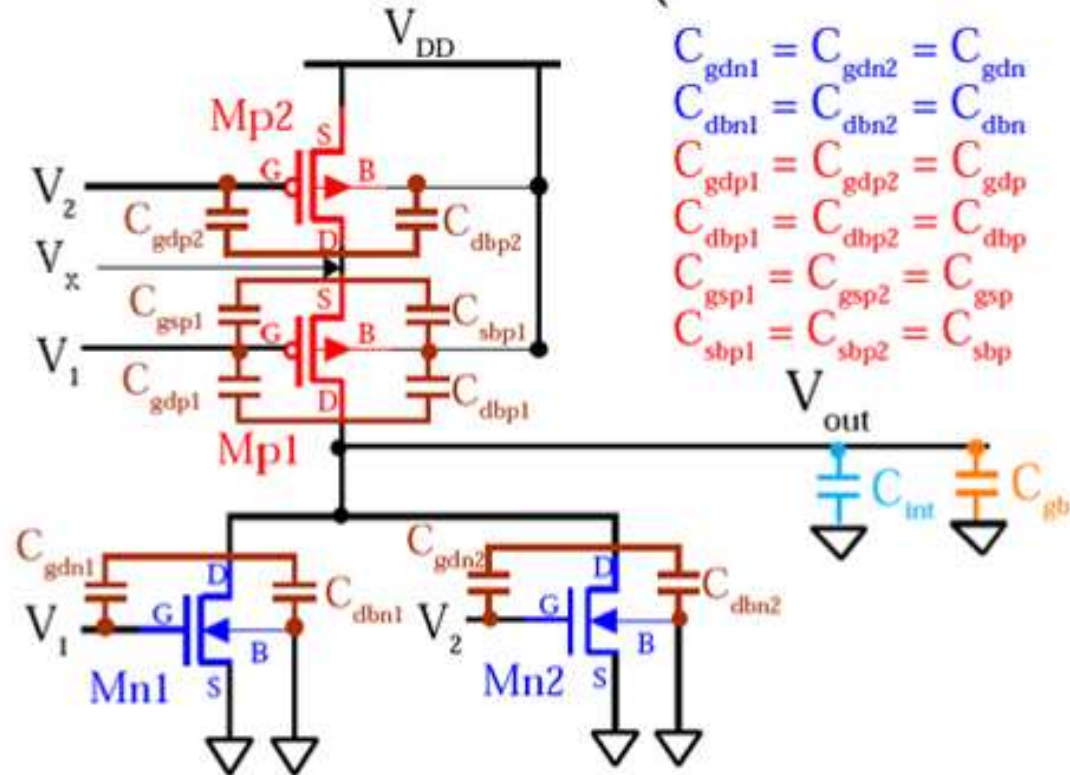

WORST CASE for PULL-UP $\Rightarrow V_1 = 0, V_2 = V_{DD} \rightarrow 0$ & $V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-NR2}} \approx 2C_{dbn} + 2C_{dbp} + C_{sbp} + C_{int} + C_{gb} = 2C_{dbn} + 3C_{dbp} + C_{int} + C_{gb}$$

WORST CASE for PULL-DOWN $\Rightarrow V_1 = 0, V_2 = 0 \rightarrow V_{DD}$ & $V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-NR2}} \approx 2C_{dbn} + 2C_{dbp} + C_{sbp} + C_{int} + C_{gb} = 2C_{dbn} + 3C_{dbp} + C_{int} + C_{gb}$$

NRn: $C_{\text{load-NRn}} \approx nC_{dbn} + (2n-1)C_{dbp} + C_{int} + C_{gb}$

NR2:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(NR2) = V_{DD}/2 \Rightarrow k_p = 4k_n$$

2. Propagation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-NR2} \approx \frac{C_{load-NR2}}{2k_n(V_{DD}-V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD}-V_{T0n}} + \ln \left(\frac{4(V_{DD}-V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NR2} \approx \frac{C_{load-NR2}}{\frac{k_p(V_{DD}-|V_{T0p}|)}{2}} \left[\frac{2|V_{T0p}|}{V_{DD}-|V_{T0p}|} + \ln \left(\frac{4(V_{DD}-|V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

NRn:


1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(NRn) = V_{DD}/2 \Rightarrow k_p = n^2k_n$$

2. Propagation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-NRn} \approx \frac{C_{load-NRn}}{nk_n(V_{DD}-V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD}-V_{T0n}} + \ln \left(\frac{4(V_{DD}-V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NRn} \approx \frac{C_{load-NRn}}{\frac{k_p(V_{DD}-|V_{T0p}|)}{n}} \left[\frac{2|V_{T0p}|}{V_{DD}-|V_{T0p}|} + \ln \left(\frac{4(V_{DD}-|V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

 


CMOS ND2

$$V_{th}(ND2) \Rightarrow V_1 = V_2 = V_{out}$$

$$V_{th}(INV) = V_{in} = V_{out}$$


 
$$\frac{k_{pEQV}}{k_{nEQV}} = 4 \frac{k_p}{k_n}$$



$$V_{th}(NAND2) = \frac{V_{Tn} + 2\sqrt{\frac{k_p}{k_n}}(V_{DD} + V_{Tp})}{1 + 2\sqrt{\frac{k_p}{k_n}}}$$


$$V_{th}(INV) = \frac{V_{Tn} + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}(V_{DD} + V_{Tp})}{1 + \sqrt{\frac{k_{pEQV}}{k_{nEQV}}}}$$

Symmetrical EQUIV INV

$$k_{pEQV} = k_{nEQV} \text{ and } V_{Tn} = |V_{Tp}| \Rightarrow V_{th}(INV) = V_{DD}/2$$

$$V_{th}(ND2) = V_{DD}/2 \Rightarrow k_n = 4k_p$$

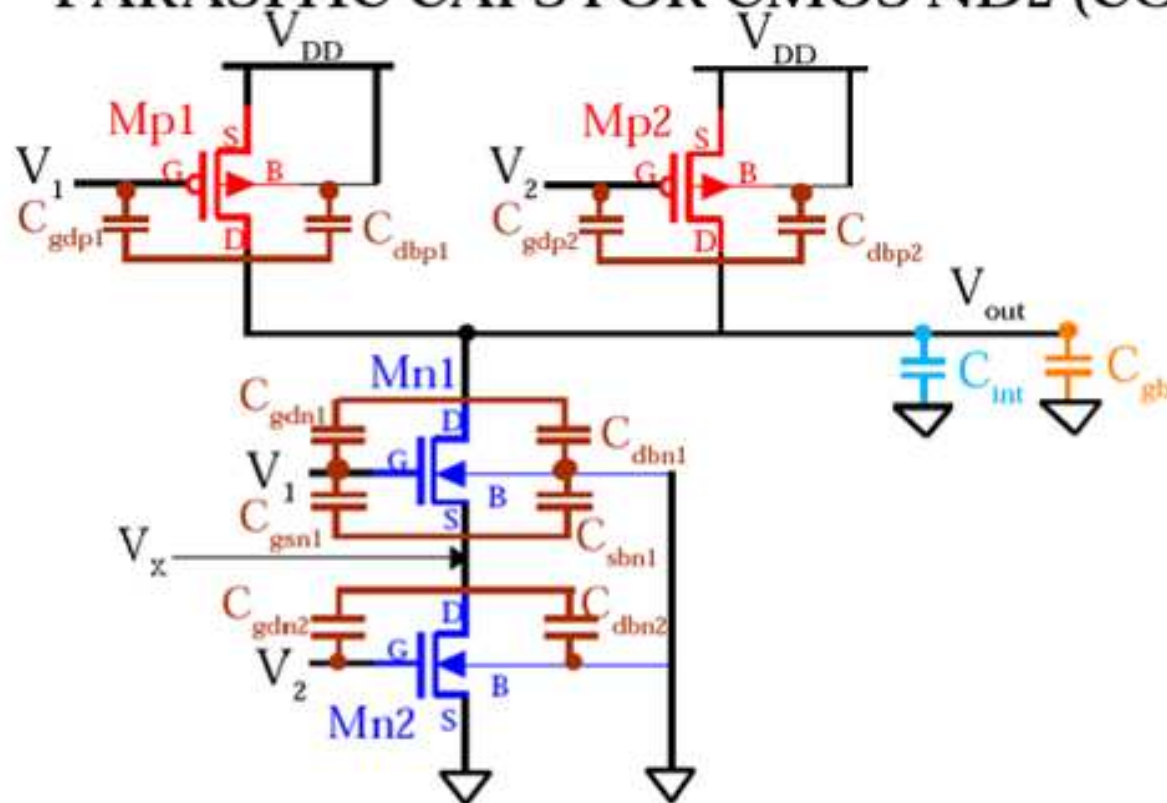PARASITIC CAPS FOR CMOS ND2 (CONSERVATIVE) 25



$$\begin{aligned}
 C_{gdn1} &= C_{gdn2} = C_{gdn} \\
 C_{dbn1} &= C_{dbn2} = C_{dbn} \\
 C_{gdp1} &= C_{gdp2} = C_{gdp} \\
 C_{dbp1} &= C_{dbp2} = C_{dbp} \\
 C_{gsn1} &= C_{gsn2} = C_{gsn} \\
 C_{sbn1} &= C_{sbn2} = C_{sbn}
 \end{aligned}$$

WORST CASE for PULL-UP $\Rightarrow V_1 = V_{DD}, V_2 = V_{DD} \rightarrow 0$ & $V_x = \text{low} \rightarrow \text{high}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{\text{int}} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{\text{int}} + C_{gb}$$

WORST CASE for PULL-DOWN $\Rightarrow V_1 = V_{DD}, V_2 = 0 \rightarrow V_{DD}$ & $V_x = \text{high} \rightarrow \text{low}$

$$C_{\text{load-ND2}} \approx 2C_{dbn} + C_{sbn} + 2C_{dbp} + C_{\text{int}} + C_{gb} = 3C_{dbn} + 2C_{dbp} + C_{\text{int}} + C_{gb}$$

NDn: $C_{\text{load-NDn}} \approx (2n-1)C_{dbn} + nC_{dbp} + C_{\text{int}} + C_{gb}$

ND2:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(ND2) = V_{DD}/2 \Rightarrow k_n = 4k_p$$

2. Propagation delay τ_{PHL} or τ_{PLH} :

$$\tau_{PHL-ND2} \approx \frac{C_{load-ND2}}{\frac{k_n(V_{DD}-V_{T0n})}{2}} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-ND2} \approx \frac{C_{load-ND2}}{2k_p(V_{DD}-|V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

NDn:

1. Symmetric Inverter $V_{th} = V_{DD}/2$:

$$V_{th}(NDn) = V_{DD}/2 \Rightarrow k_n = n^2k_p$$

2. Propagation delay τ_{PHL} or τ_{PLH} :





$$\tau_{PHL-NDn} \approx \frac{C_{load-NDn}}{\frac{k_n(V_{DD}-V_{T0n})}{n}} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PLH-NDn} \approx \frac{C_{load-NDn}}{nk_p(V_{DD}-|V_{T0p}|)} \left[\frac{2|V_{T0p}|}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{4(V_{DD} - |V_{T0p}|)}{V_{DD}} - 1 \right) \right]$$

TYPICAL CMOS NAND AND NOR DELAYS

Delays for a Family of **NAND & NOR** gates

    1. $W_n = 6.4 \mu\text{m}$, $L_n = 1 \mu\text{m}$, and $W_p = 12.8 \mu\text{m}$, $L_p = 1 \mu\text{m}$.
2. $t_{\text{input-rise/fall}} = 0.1 \text{ ns}$ and $C_{\text{load}} = 0 \rightarrow 1 \text{ pF}$.





NR2 Layout Example


29

COLOR LEGEND

  
- n-Well
- p-Well
- n⁺
- Polysilicon
- p⁺
- Gate Oxide
- Field Oxide
- Metal 1
- Metal 2
- Metal 3
- Contact/via



STICK DIAGRAM →

 


ND2 Layout Example

 

COLOR LEGEND 30

 
- n-Well
- p-Well
- n⁺
- Polysilicon
- p⁺
- Gate Oxide
- Field Oxide
- Metal 1
- Metal 2
- Metal 3
- Contact/via




COMPLEX LOGIC GATES

$$Z = \overline{A(D + E) + BC}$$

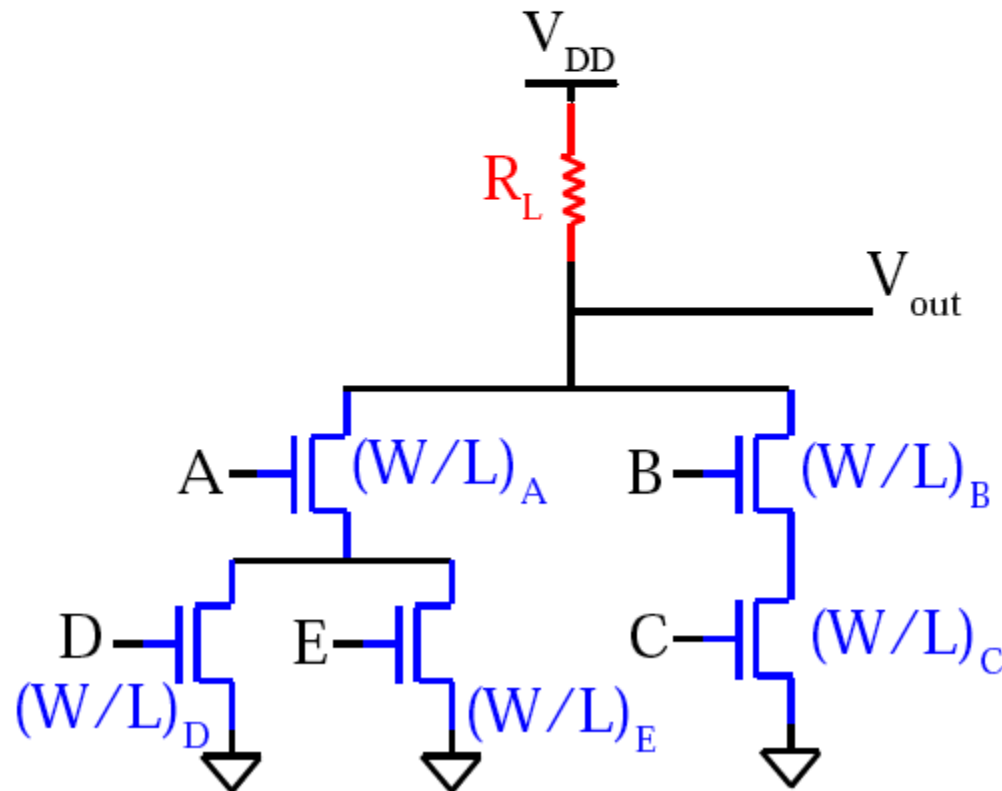- “OR” OPS PERFORMED BY PARALLEL CONECTED DRIVERS.
- “AND” OPS PERFORMED BY SERIES CONNECTED DRIVERS.
- “INVERSION” IS PROVIDED BY NATURE OF MOS CIRCUIT OP.




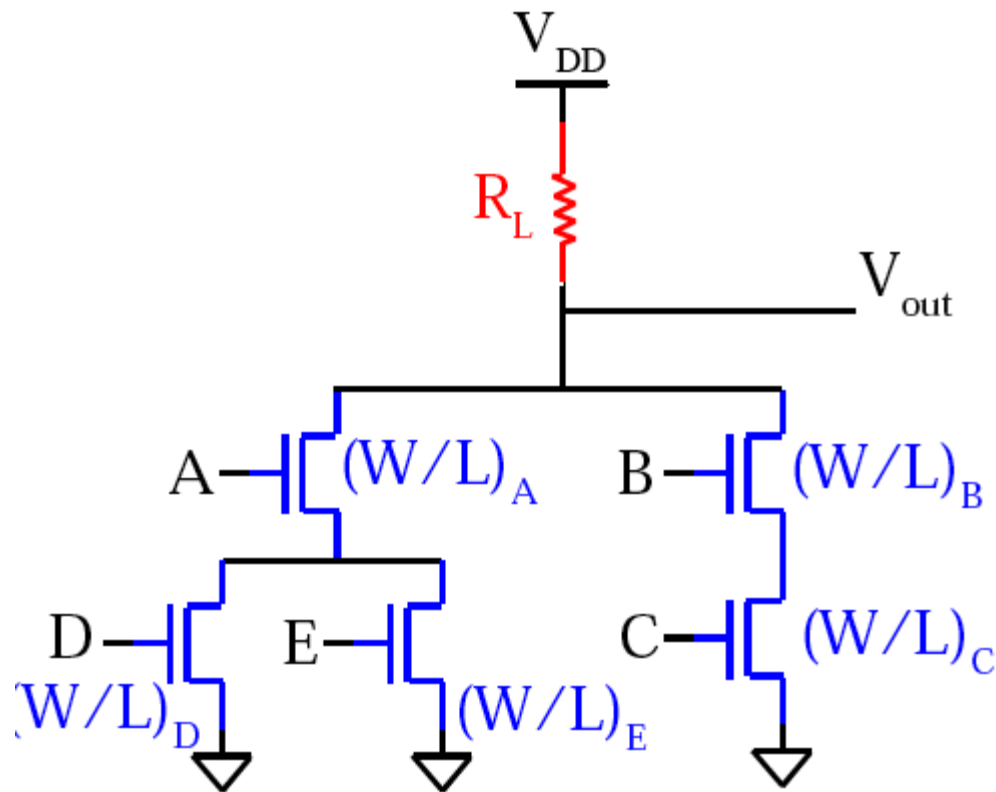

ON Drivers	Out-GND Path
A-D	Class 1
A-E	Class 1
B-C	Class 1
A-D-E	Class 2
A-D-B-C	Class 3
A-E-B-C	Class 3
A-D-E-B-C	Class 4
$G1 < G2 < G3 < G4$ $V_{OL1} > V_{OL2} > V_{OL3} > V_{OL4}$	

EQV INVERTER (for case G4 where $A = B = C = D = E = 1$)
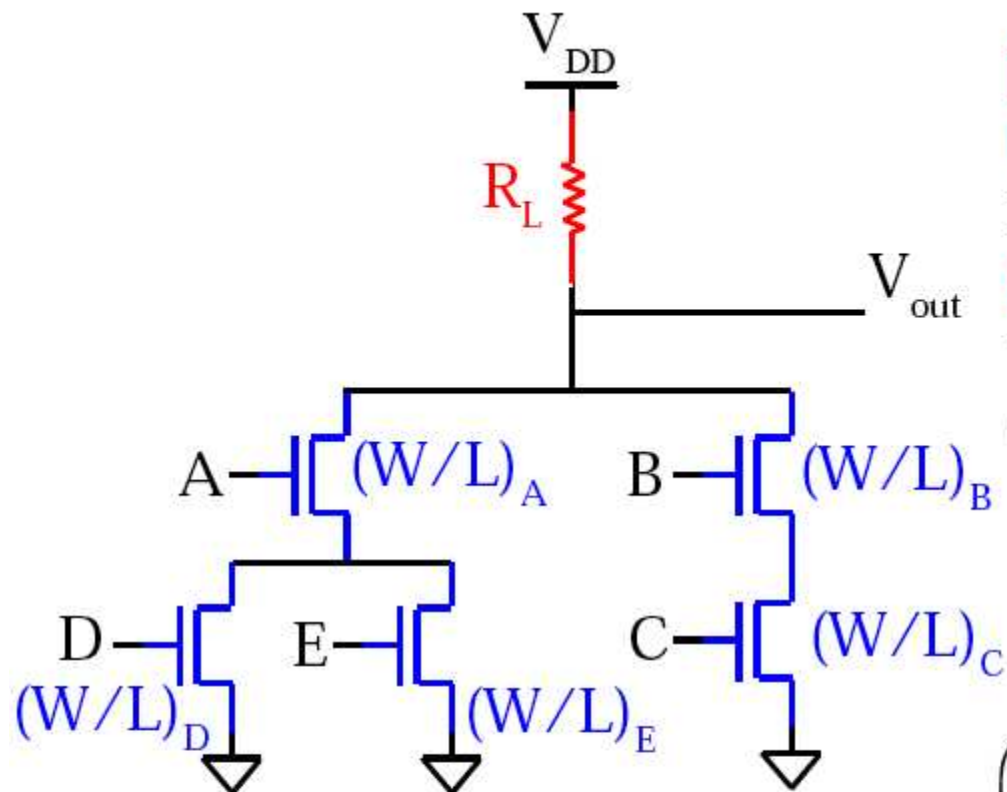
$$\left(\frac{W}{L}\right)_{\text{EQV}} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_B} + \frac{1}{\left(\frac{W}{L}\right)_C}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_A} + \frac{1}{\left(\frac{W}{L}\right)_D + \left(\frac{W}{L}\right)_E}}$$



$$\left(\frac{W}{L}\right)_{\text{EQV-ND2}} = \frac{1}{2} \left(\frac{W}{L}\right)$$

DESIGN STRATEGY:


1. Identify all WORST CASE Paths (e.g. Class 1).
2. Determine nMOS transistor sizes such that each Class 1 path has $(W/L)_{\text{EQV}}$

$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_D = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$


$$\left(\frac{W}{L}\right)_A = \left(\frac{W}{L}\right)_E = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$

$$\left(\frac{W}{L}\right)_B = \left(\frac{W}{L}\right)_C = 2 \left(\frac{W}{L}\right)_{\text{EQV}}$$



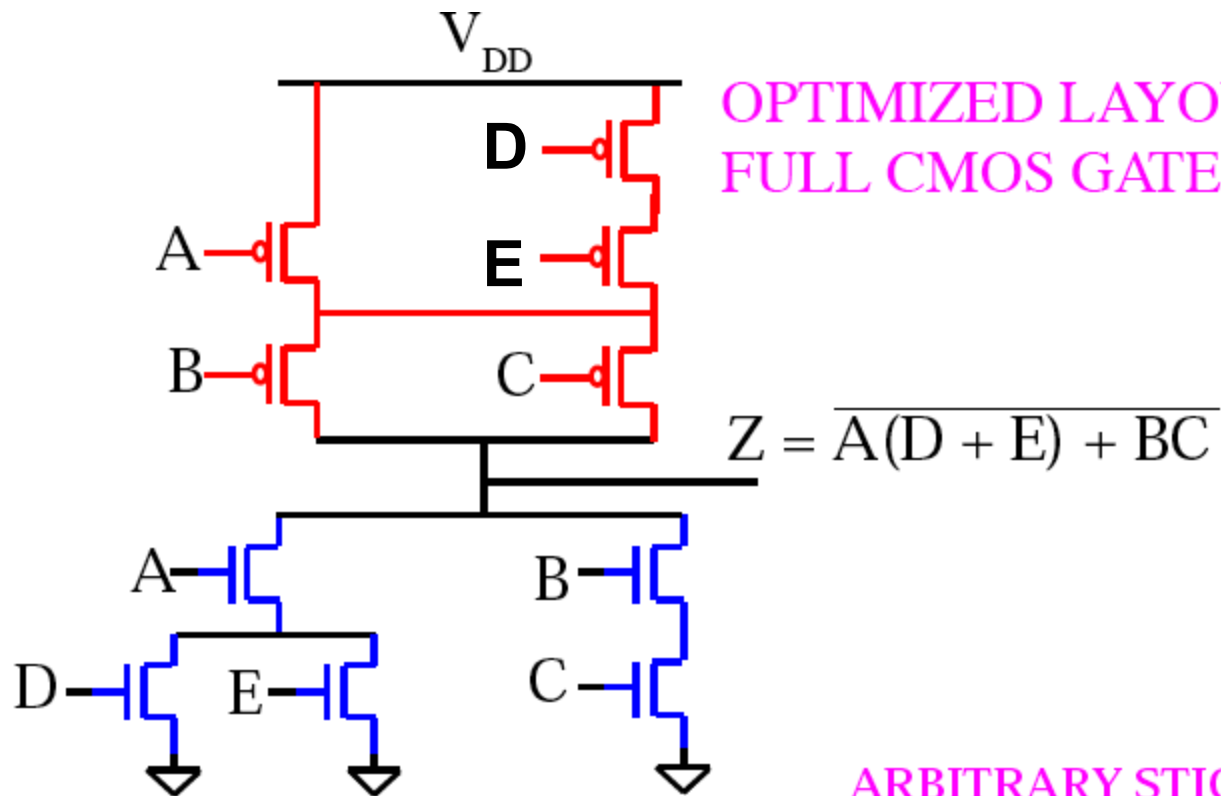
OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES



ARBITRARY STICK LAYOUT




 


   OPTIMIZED LAYOUT OF COMPLEX FULL CMOS GATES



ARBITRARY ORDERING OF GATE COLUMNS


36

    

Euler path - connected sequence of edges




n, p diffusions for common **Euler paths** have layouts with no diffusion breaks.

MINIMIZE NUMBER OF DIFFUSION BREAKS

 


COMMON
EULER PATH:
E-D-A-B-C


Is A-D-E-C-B a
common Euler
path?

   

Arbitrary Stack

 


Optimized Stack

 

ALGORYTHYM FOR LINE OF GATES LAYOUT STYLE

1. Find all Euler paths that cover the graph.
2. Find common n- and p- Euler paths.
3. If no Euler paths are found in step 2, break the gate in the minimum number of places that to achieve step 2 with separate common Euler paths.


FULL CMOS XOR GATE

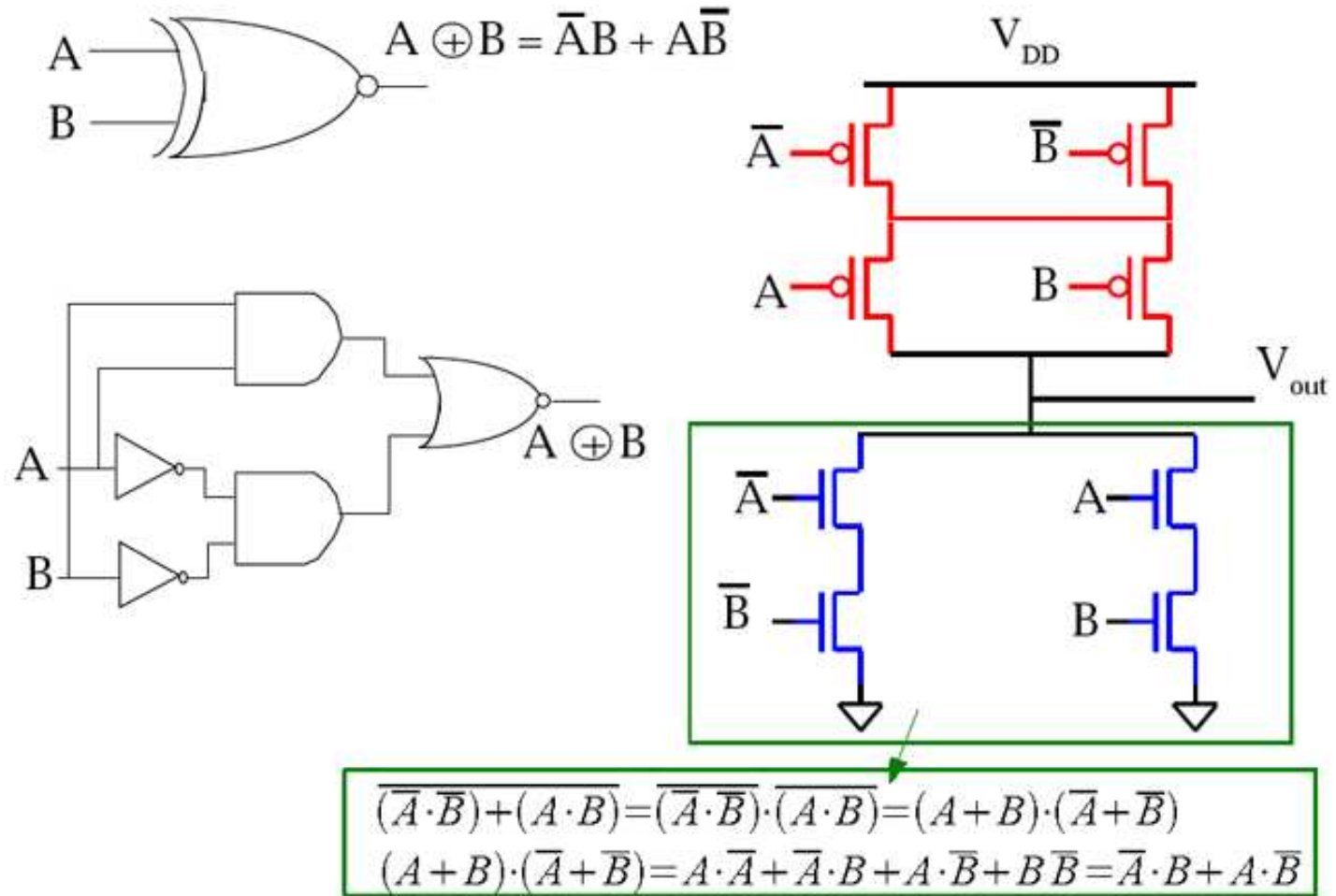



AOI & OAI GATES

AOI -> AND-OR-INVERT (for SUM - of - PRODUCTS Realization)

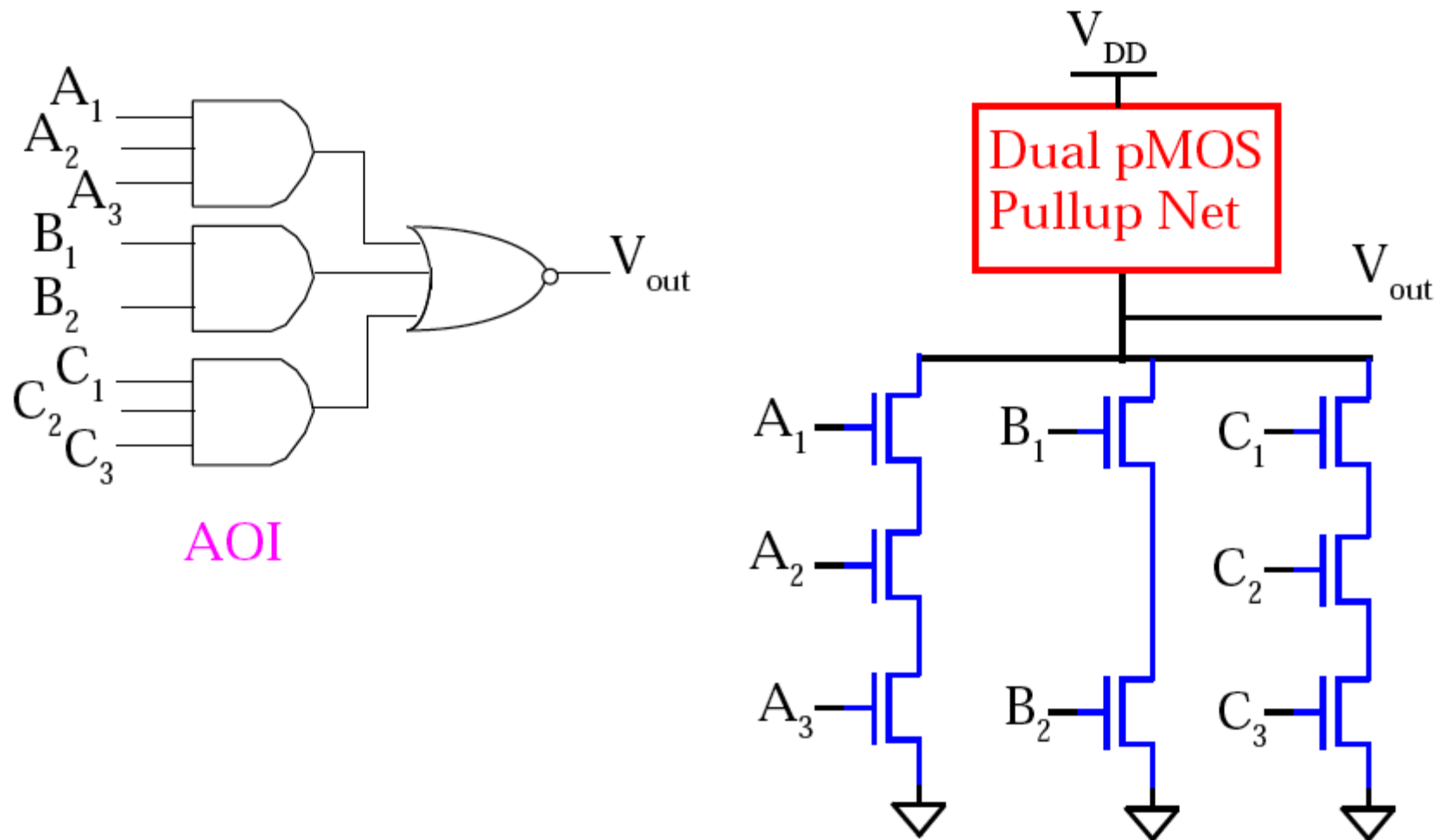
OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)



  OAI -> OR-AND-INVERT (for PRODUCT - of - SUMS Realization)




Pseudo-nMOS OAI Realization

 

CMOS Transmission Gates (TGs) & TG Logic

SYMBOLS

 



SWITCH CHARACTERISTICS

Input

Output

0 a — o —▶— o — b Strong 0

1 a — o —▶— o — b Strong 1

  

$$R_{eqn} = \frac{V_{DD} - V_{out}}{I_{DSn}}$$

$$R_{eqp} = \frac{V_{DD} - V_{out}}{I_{SDp}}$$

$$R_{eqTOT} = R_{eqn} || R_{eqp}$$

REGION 1:
nMOS: SAT
pMOS: SAT

$$R_{eqn} = \frac{2(V_{DD} - V_{out})}{k_n (V_{DD} - V_{out} - V_{Tn})^2}$$

$$R_{eqp} = \frac{2(V_{DD} - V_{out})}{k_p (V_{DD} - |V_{Tp}|)^2}$$

REGION 2
nMOS: SAT
pMOS: LIN

$$R_{eqn} = \frac{2(V_{DD} - V_{out})}{k_n (V_{DD} - V_{out} - V_{Tn})^2}$$


$$R_{eqp} = \frac{2(V_{DD} - V_{out})}{k_p [2(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2]}$$



$$= \frac{2}{k_p [2(V_{DD} - |V_{Tp}|) - (V_{DD} - V_{out})]}$$

REGION 3
nMOS: OFF
pMOS: LIN

$$R_{eqn} = \infty$$

$$R_{eqp} = \frac{2}{k_p [2(V_{DD} - |V_{Tp}|) - (V_{DD} - V_{out})]}$$

 

  


TRANSMISSION GATE LAYOUTS



Simple and small,
but no metal lines
can pass
horizontally



 poly used to achieve
horizontal metal1
transparency




metal2 used to
achieve
horizontal metal1
transparency


Routing Gate Signals to Transmission Gate




horizontal, via
metal1

 


vertical, via poly

 

 vertical, via metal1 straps
metal2 used to achieve vertical
metal1 transparency




2-INPUT MULTIPLEXER

 


$$\text{output} = A.s + B.\bar{s}$$

A	B	s	\bar{s}	output
x	0	0	1	0 (B)
x	1	0	1	1 (B)
0	x	1	0	0 (A)
1	x	1	0	1 (A)

 XOR (COMPLEMENTARY PASS-TRANSISTOR LOGIC OR CPL)



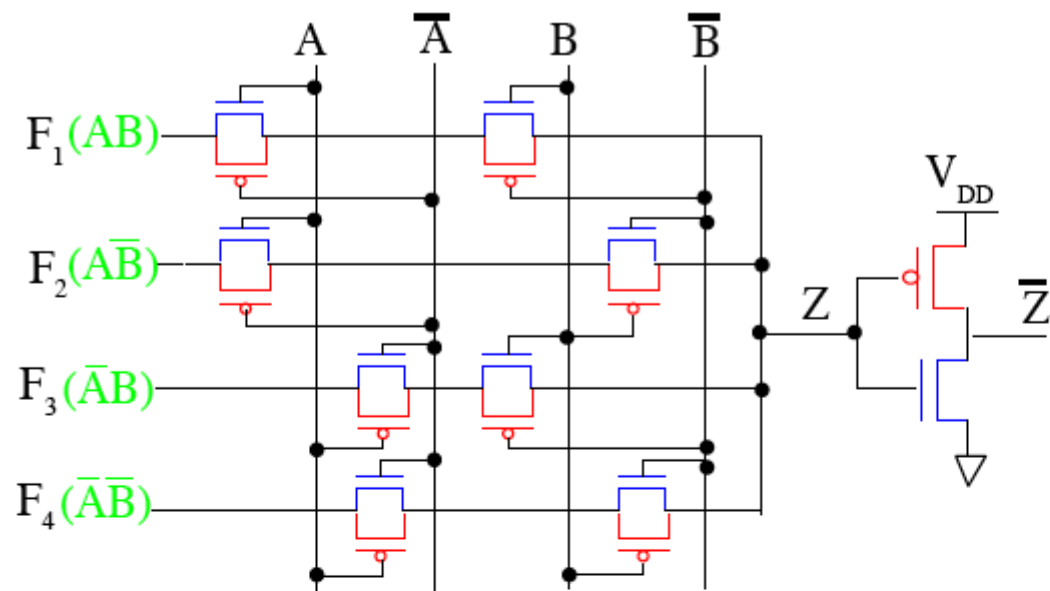

SOME OF THE FUNCTIONS REALIZED BY THE BOOLEAN FUNCTION UNIT (CPL)

OPERATION (Z)	F_1	F_2	F_3	F_4
NOR(A,B)	0	0	0	1
XOR(A,B)	0	1	1	0
NAND(A,B)	0	1	1	1
AND(A,B)	1	0	0	0
OR(A,B)	1	1	1	0