

# **CSE 463-563: Digital Integrated Circuits Design and Architecture**

***Prof. Darko Ivanovich***

## **Exam 2: Inverters and Combinational Logic Circuits**

(Take home exam, Open book, Open notes, Internet search, Calculator or Wolfram-Alpha app are allowed)

Due April 18<sup>th</sup>, 2023

*Attempt all questions. Show all calculations to obtain partial credits. If you run out of time, outline how you would approach the problem.*

*Total possible points: 200 for CSE463 students (Problems 1, 2, and 3)  
270 for CSE563 students (Problems 1, 2, 3, and 4)*

*My phone number for any question you have is 314-537-4124.  
Please text me and I will answer quickly.*

**Student name: Byeongchan Gwak**

***CSE463 students will work on Problems P1, P2 and P3***

***CSE563 students will work on Problems P1, P2, P3 and P4***

Problem P1. (50pts)

Design a 3-input CMOS NOR gate with logic threshold voltage of  $V_{DD}/3$ .

- (a) Find ratio  $k_p/k_n$  for  $V_{TH} = V_{DD}/3$ . (10pts)
- (b) The 3-input CMOS NOR gate should have a maximum fall time  $\tau_{fall}$  of 1ns for 100fF load capacitance. Use this fall time requirement to determine proper size of nMOS transistors  $(W/L)_n$ . (15pts)
- (c) From (a) and (b) determine proper size of pMOS transistors  $(W/L)_p$ . (15pts)
- (d) Select  $W_n$ ,  $L_n$ ,  $W_p$  and  $L_p$  using calculations from (b) and (c). (10pts)

Assume  $k_n' = 100\mu A/V^2$ ,  $k_p' = 100\mu A/V^2$ ,  $V_{DD} = 5V$ ,  $V_{T0n} = 1V$ ,  $|V_{T0p}| = 1V$ ,  $\gamma = 0$  and  $\lambda = 0 V^{-1}$ .

1. (a)

Since  $V_{th} = \frac{V_{DD}}{3}$ ,  
 we have  $K_{p,eq} = \frac{K_p}{3}$   
 $K_{n,eq} = 3K_n$

$$V_{th} = \frac{V_{To,n} + \sqrt{\frac{K_{p,eq}}{K_{n,eq}}} (V_{DD} + V_{To,p})}{1 + \sqrt{\frac{K_{p,eq}}{K_{n,eq}}}}$$

$$V_{th} = \frac{V_{DD}}{3} = \frac{5}{3} = \frac{1 + \sqrt{\frac{1}{9} \cdot \frac{K_p}{K_n}} (5-1)}{1 + \sqrt{\frac{1}{9} \cdot \frac{K_p}{K_n}}}$$

And we have  $K_n' = K_p'$ ,

$$\frac{5}{3} = \frac{1 + \frac{4}{3} \sqrt{\frac{K_p}{K_n}}}{1 + \frac{1}{3} \sqrt{\frac{K_p}{K_n}}}$$

$$\boxed{\frac{K_p}{K_n} = 0.73469}$$

$$(b) \ln s > T_{fall} = \frac{C_{load}}{3K_n(V_{DD} - V_{To,n})} \left[ \frac{2(V_{To,n} - 0.1V_{DD})}{V_{DD} - V_{To,n}} + \ln \left( \frac{2(V_{DD} - V_{To,n})}{0.1V_{DD}} - 1 \right) \right]$$

$$\ln s > \frac{100 \times 10^{-15}}{3 \times 100 \times 10^{-6} \left( \frac{W}{L} \right)_n (5-1)} \left[ \frac{2(1-0.5)}{5-1} + \ln \left( \frac{2(5-1)}{0.5} - 1 \right) \right]$$

$$\ln s > \frac{10^{-9}}{3 \times 4 \times \left( \frac{W}{L} \right)_n} \left[ \frac{1}{4} + \ln(15) \right]$$

$$\boxed{\left( \frac{W}{L} \right)_n > 0.2465}$$

(c) From the answers above.

$$k_p = 0.73469 k_n, \quad \left(\frac{W}{L}\right)_n > 0.2465$$

I will choose  $L_n = 600 \text{ nm}$   $W_n = 1800 \text{ nm}$ .

$$k_p = \left(\frac{W}{L}\right)_p = 0.73469 \times \frac{1800}{600} = 2.204$$

(d)  $L_n = 600 \text{ nm}$ ,  $W_n = 1800 \text{ nm}$ ,  $L_p = 600 \text{ nm}$

$$k_p = \left(\frac{W}{L}\right)_p = 2.204$$

$$\frac{W_p}{600} = 2.204$$

$$W_p = 1322$$

so,  $W_p = 1322 \text{ nm}$

Hence.

$$L_n = 600 \text{ nm}, \quad W_n = 1800 \text{ nm}, \quad L_p = 600 \text{ nm}, \quad W_p = 1322 \text{ nm}.$$


Problem P2. (70pts)

Consider the following function:  $Z = (A + B + C)(D + E)F$ .

- (a) Draw the pMOS and nMOS CMOS transistors schematic of the function  $Z$ . Assume that all signals and their respective inverse signals are available for the design. (10 pts)
- (b) If all transistors are implemented with  $W/L = 1$ ,  $k_p' = k_n' = 100\mu\text{A}/\text{V}^2$ ,  $V_{DD} = 5\text{V}$ ,  $V_{T0n} = 1\text{V}$  and  $|V_{T0p}| = 1\text{V}$ , what is the value of the logic threshold,  $V_{TH}$ , when all inputs are connected to  $V_{TH}$ ? (10 pts)
- (c) Which transitions will have the longest rise and fall times? (10 pts)
- (d) Calculate the longest rise time for  $C_{load}$  of 100fF. (20 pts)
- (e) What is the common Euler path for the pMOS and nMOS network of transistors? Draw the optimized stick-diagram layout. (20 pts)

2 (a)  $Z = (A+B+C)(D+E)F$
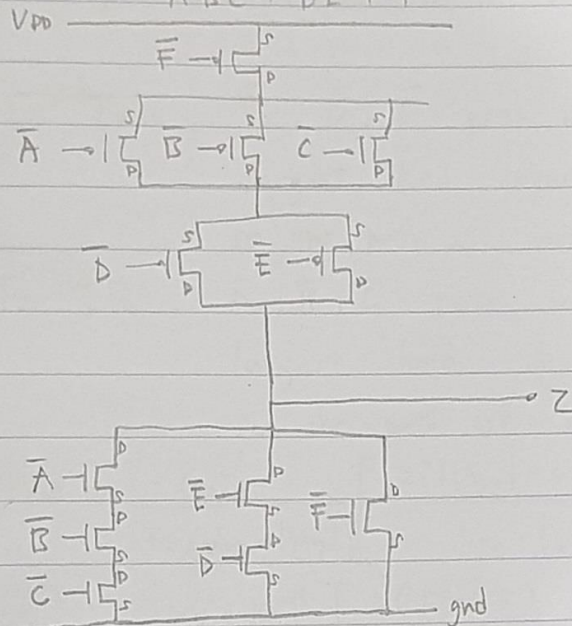
$$\bar{Z} = \overline{A\bar{B}\bar{C} + D\bar{E} + \bar{F}}$$



$$(b) \left(\frac{W}{L}\right)_{n,eq} = \left(\frac{W}{L}\right)_{\bar{F}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_{\bar{F}}} + \frac{1}{\left(\frac{W}{L}\right)_D}} + \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_{\bar{A}}} + \frac{1}{\left(\frac{W}{L}\right)_{\bar{B}}} + \frac{1}{\left(\frac{W}{L}\right)_{\bar{C}}}}$$

$$= 1 + \frac{1}{1+1} + \frac{1}{1+1+1} = 1 + \frac{1}{2} + \frac{1}{3} = \frac{6+3+2}{6} = \frac{11}{6}$$

$$\left(\frac{W}{L}\right)_{p,eq} = \frac{1}{\frac{1}{\left(\frac{W}{L}\right)_{\bar{F}}} + \frac{1}{\left(\frac{W}{L}\right)_{\bar{E}} + \left(\frac{W}{L}\right)_D} + \frac{1}{\left(\frac{W}{L}\right)_{\bar{A}} + \left(\frac{W}{L}\right)_{\bar{B}} + \left(\frac{W}{L}\right)_{\bar{C}}}}$$

$$= \frac{1}{1 + \frac{1}{2} + \frac{1}{3}} = \frac{1}{\frac{11}{6}} = \frac{6}{11}$$

$$V_{th} = \frac{V_{To,n} + \sqrt{\frac{K_{p,eq}}{K_{n,eq}}} (V_{DD} + V_{To,p})}{1 + \sqrt{\frac{K_{p,eq}}{K_{n,eq}}}}$$

$$= \frac{1 + \sqrt{\frac{6/11}{11/6}} (5 - 1)}{1 + \sqrt{\frac{6/11}{11/6}}} = \frac{1 + 4\sqrt{\frac{6^2}{11^2}}}{1 + \sqrt{\frac{6^2}{11^2}}} = \boxed{2.0588 V}$$



(c) In order to have largest rise, fall time, largest load capacitance is needed.

For  $T_{rise}$ ,  $\bar{B}, \bar{D}, \bar{F}$  path will have the largest load capacitance.

so the path will have longest rise time




For  $T_{fall}$ ,  $\bar{A}, \bar{B}, \bar{C}$  path will have the largest load capacitance.

so the path will have longest fall time.

$$\begin{aligned}
 (d) T_{rise} &= \frac{C_{load}}{K_{p,eff}(V_{DD} - |V_{Top}|)} \left[ \frac{2(|V_{Top}| - 0.1V_{DD})}{V_{DD} - |V_{Top}|} + \ln \left( \frac{2(V_{DD} - |V_{Top}|)}{0.1V_{DD}} - 1 \right) \right] \\
 &= \frac{100 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{11} \times 4} \left[ \frac{2(1 - 0.5)}{(5 - 1)} + \ln \left( \frac{2(5 - 1)}{0.5} - 1 \right) \right] \\
 &= \frac{11}{24} \times 10^{-9} \times \left( \frac{1}{4} + \ln(15) \right) = 1.355 \times 10^{-9}
 \end{aligned}$$

$$= 1.355 \text{ ns}$$

(e)

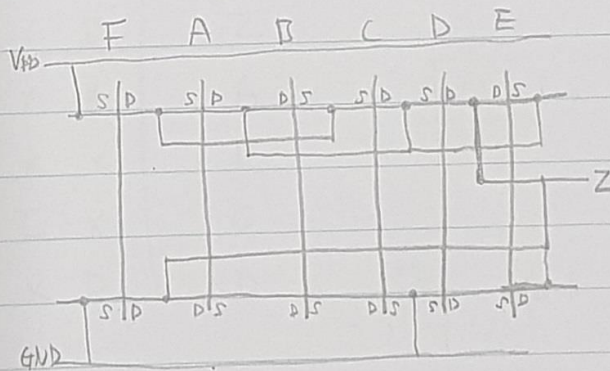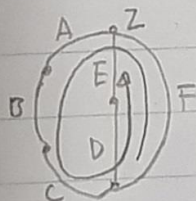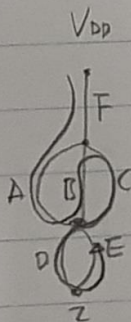


Euler Path =  $F \rightarrow A \rightarrow B \rightarrow C \rightarrow D \rightarrow E$

Problem P3. (80 pts)

You need to design a 4-to-1 multiplexer.

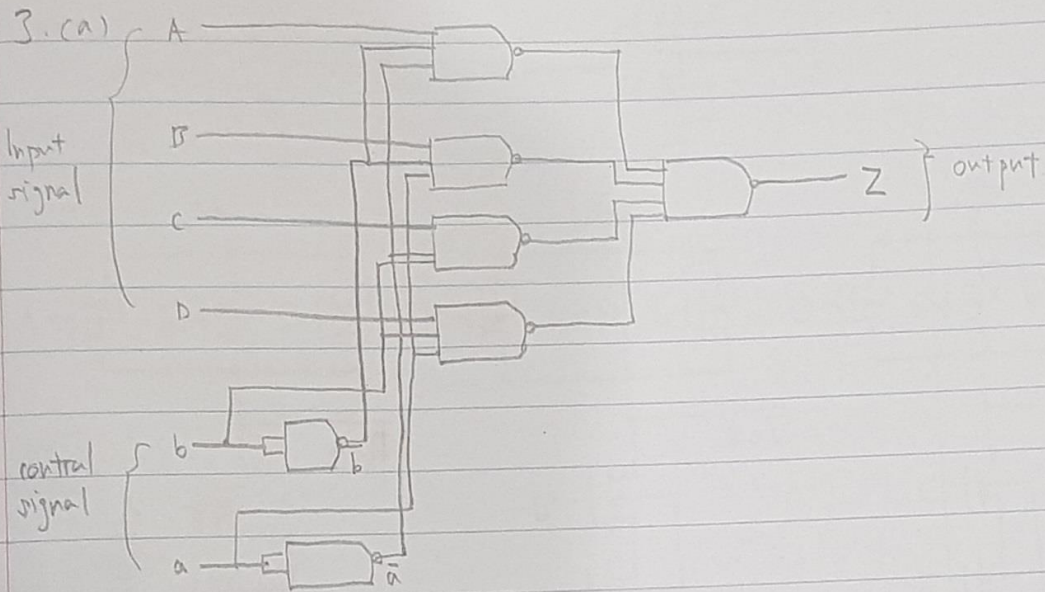
- (a) Draw a logic gate design of your 4-to-1 multiplexer design. Specify all logic gates, input signals, control signals and output signal connections in your gate level design. (20pts)
- (b) Define Truth Table and Logic Equation of your 4-to-1 multiplexer design using input signals, control signals and output signal. (20pts)
- (c) Draw your detailed pMOS and nMOS transistor level design. You need to show how you would connect all pMOS and nMOS transistors' drains, sources, gates and bulks inside your detailed design. Show the multiplexer's input signals, control signals and output signal connected in your transistor level design. You should use your logic gate design from the part (a) to design your transistor level design. (40pts)





$$\begin{aligned}
 \text{b) } Q &= (\overline{A\bar{a}\bar{b}})(\overline{B\bar{a}\bar{b}})(\overline{C\bar{a}\bar{b}})(\overline{D\bar{a}\bar{b}}) \\
 &= (\bar{A} + a + b)(\bar{B} + \bar{a} + b)(\bar{C} + a + \bar{b})(\bar{D} + \bar{a} + \bar{b}) \\
 &= \bar{a}\bar{b}A + a\bar{b}B + \bar{a}bC + abD
 \end{aligned}$$

control signals		data signals				Output
a	b	A	B	C	D	Z
0	0	A	x	x	x	A
1	0	x	B	x	x	B
0	1	x	x	C	x	C
1	1	x	x	x	D	D

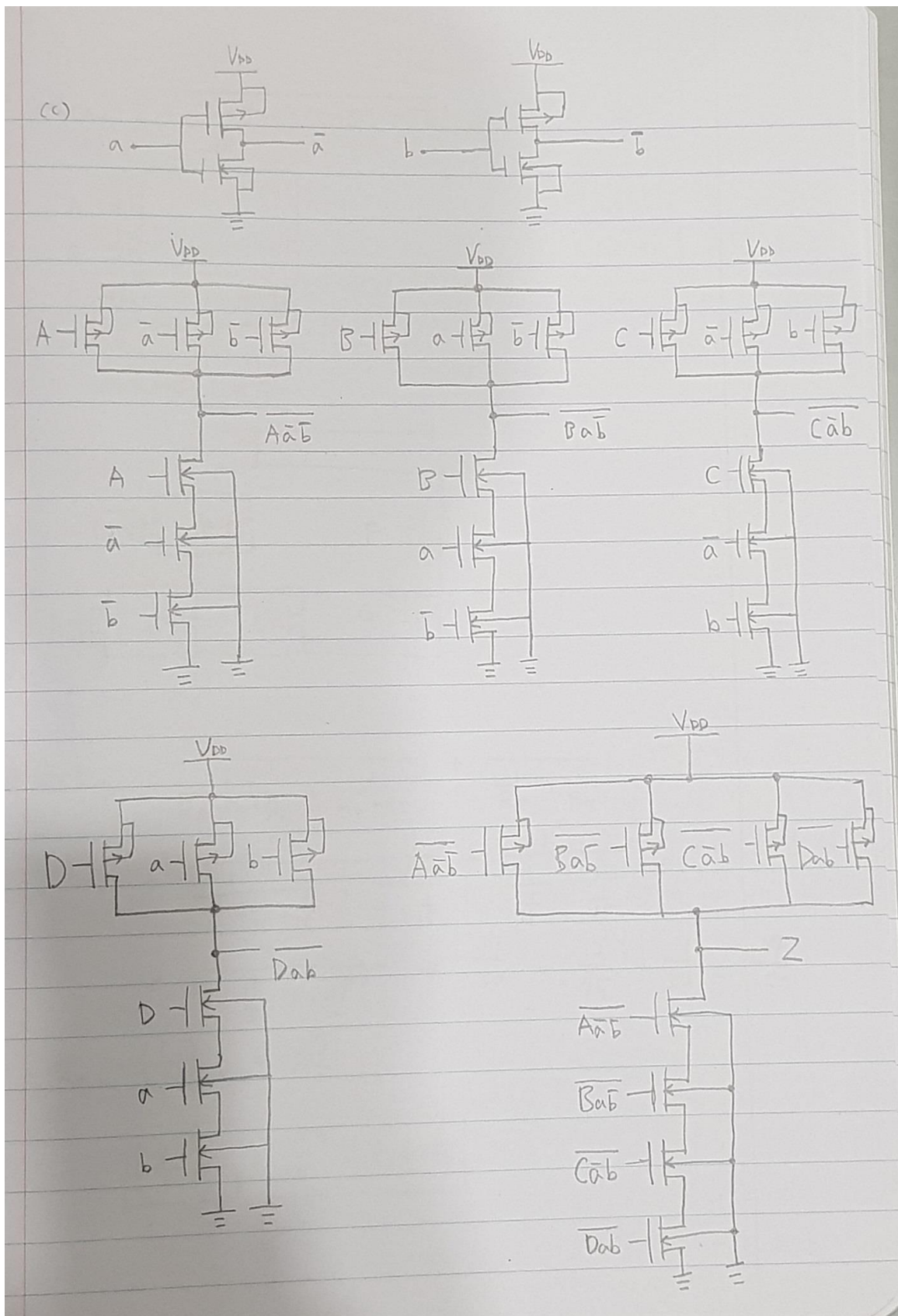


Problem P4. (70 pts)

Consider the following function:  $Z = \overline{(A + B + C)(D + E)} + FG$ .

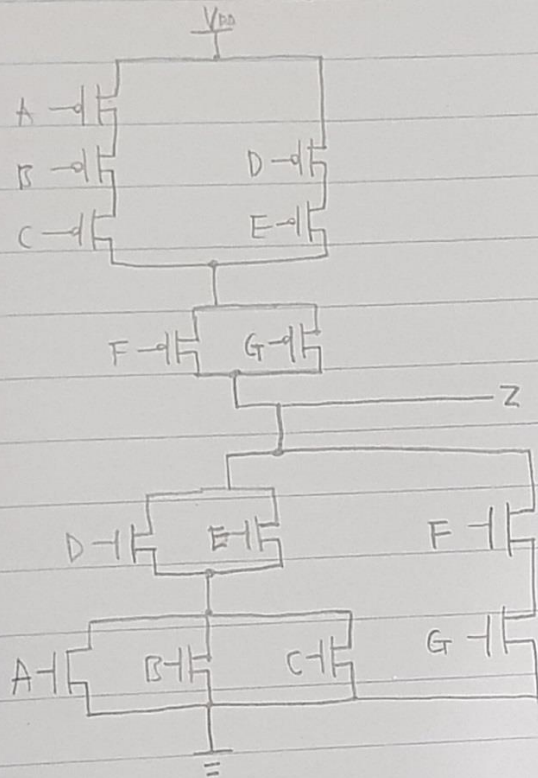- (a) Draw the pMOS and nMOS CMOS transistors schematic of the function  $Z$ . Assume that all signals and their respective inverse signals are available for the design. (10 pts)
- (b) If  $(W/L)_p = 15$  determine  $(W/L)_{p,eq}$  for the design. (30 pts)
- (c) If  $(W/L)_n = 10$  determine  $(W/L)_{n,eq}$  for the design. (30 pts)

$$4(a) Z = \overline{(A+B+C)(D+E) + FG}$$



$$\begin{aligned} (b) R_{eq} &= \frac{1}{\frac{1}{R_A + R_B + R_C} + \frac{1}{R_D + R_E}} + \frac{1}{\frac{1}{R_F} + \frac{1}{R_G}} \\ &= \frac{1}{\frac{1}{15} + \frac{1}{15} + \frac{1}{15}} + \frac{1}{\frac{1}{15} + \frac{1}{15}} = \\ &= \frac{1}{\frac{15}{3} + \frac{15}{2}} + \frac{1}{30} = \frac{6}{75} + \frac{1}{30} = \frac{17}{150} \end{aligned}$$

$$R_{eq} = \left( \frac{L}{W} \right)_{p,eq} = \frac{17}{150}$$

$$\left( \frac{W}{L} \right)_{p,eq} = \frac{150}{17} = 8.8235$$



$$\begin{aligned}
 \frac{1}{R_{eq,n}} &= \frac{1}{\frac{1}{R_A} + \frac{1}{R_B} + \frac{1}{R_C}} + \frac{1}{\frac{1}{R_D} + \frac{1}{R_E}} + \frac{1}{R_F + R_G} \\
 &= \frac{1}{\frac{1}{10+10+10}} + \frac{1}{\frac{1}{10+10}} + \frac{1}{\frac{1}{10} + \frac{1}{10}} \\
 &= \frac{1}{\frac{1}{30} + \frac{1}{30}} + \frac{10}{2} \\
 &= 12 + 5 = 17
 \end{aligned}$$

$$\frac{1}{R_{eq,n}} = \left( \frac{W}{L} \right)_{n,eq} = 17$$