

CSE 463-563: Digital Integrated Circuits Design and Architecture

Exam 1: MOS Transistor Theory and Inverter

(Open book, Open Notes, Calculator or Wolfram-Alpha app are allowed)

March 23th, 2023

Attempt all questions. Show all calculations to obtain partial credits. If you run out of time, outline how you would approach the problem.

*Total possible points: 200 for CSE463 students (Problems 1, 2, and 3)
270 for CSE563 students (Problems 1, 2, 3, and 4)*

*My phone number for any question you have is 314-537-4124.
Please text me and I will answer quickly.*

Student name: Byeongchan Gwak


CSE463 students will work on Problems P1, P2 and P3

CSE563 students will work on Problems P1, P2, P3 and P4

- P1. Three pieces of Si with acceptor concentration 10^{18} cm^{-3} , donor concentration 10^{15} cm^{-3} and acceptor concentration of 10^{18} cm^{-3} , respectively, are abutted. The sample temperature is $T=300\text{K}$ (60 points)
- (a) Draw the energy band diagrams before and after they are abutted. (10 points)
 - (b) Compute the built in potential for each junction. (20 points)
 - (c) Sketch and compute the depletion width for both junctions. (20 points)
 - (d) Draw the cross-section of an implementation of this device in $0.5\mu\text{m}$ CMOS process. In CMOS process, you cannot simply join these three junctions with different doping. You will have to use p^+ active, n^+ active, n -well and p -substrate to formulate this device. (10 points)

+ My solution starts.

a)

 

b)

$$V_0 = \frac{kT}{q} \ln \left(\frac{N_A N_D}{n_i^2} \right)$$

$$\frac{kT}{q} = 0.026V$$

$$N_A = 10^{18}$$

$$N_D = 10^{15}$$

$$n_i = 1.45 \cdot 10^{10}$$

$$V_0 = 0.026 \cdot \ln \left(\frac{10^{18} \cdot 10^{15}}{(1.45 \cdot 10^{10})^2} \right)$$

$$\boxed{V_0 = 0.7589V}$$

c)

$$\varepsilon = 8.85 \cdot 10^{-14} \cdot 11.7 = 1.035 \cdot 10^{-12}$$

$$q = 1.6 \cdot 10^{-19}C$$


$$W = \sqrt{\frac{2\varepsilon V_0}{q} \left(\frac{N_A + N_D}{N_A \cdot N_D} \right)}$$

$$W = \sqrt{\frac{2 \cdot 1.035 \cdot 10^{-12} \cdot 0.7589}{1.6 \cdot 10^{-19}} \left(\frac{10^{18} + 10^{15}}{10^{18} \cdot 10^{15}} \right)}$$

$$W = 0.00009913$$

$$\boxed{W = 0.9913\mu m}$$


d)

 

+ My solution ends.

P2. Consider the inverter circuit in figure P2. Assume $k_p' = 10\mu\text{A}/\text{V}^2$, $|V_{\text{top}}| = 1\text{V}$ and $\lambda = 0\text{ V}^{-1}$. (60 pts)

- Compute V_{out} if $V_{\text{in}} = 5\text{V}$. Assume that $\gamma = 0$ (10 pts)
- Compute V_{out} if $V_{\text{in}} = 0\text{V}$. Assume that $\gamma = 0$ (10 pts)
- Compute the logic threshold of the inverter, i.e. compute V_{th} . Assume that $\gamma = 0$ (10 pts)
- Draw the V_{in} vs. V_{out} curves for this circuit and clearly label V_{oh} , V_{ol} and V_{th} . (10 pts)
- How would you expect the value of V_{out} to change in (a) and (b) if $\gamma = 0.1$? (10pts)
- Assume the circuit has a logic threshold of V_{th} . Specify *two circuit modifications* that will help you increase the logic threshold value V_{th} . (10pts)

 

P.2

+ My solution starts.

a)

$$V_{in} = 5 - V_{out}$$

$$5 = 5 - V_{out}$$

$$V_{out} = 0$$


b) $V_{in} = 5 - V_{out}$, $V_{in} = 0$

$$V_{out} = 5V$$

c) $V_{th} = V_{TOP} + r(\sqrt{|1 - 2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|})$

since $r = 0$,

$$V_{th} = V_{TOP} = 1V$$

 

e) When r grows, V_{out} would increase ... (a)


when r grows, V_{out} would decrease ... (b)

f) increase the size of PMOS

decrease the size of resistor

+ My solution ends.

- P3. Consider the following circuit. The load capacitance at the output node is $C_{load}=1\text{pF}$. Use voltage values from P2 in this problem. (80 pts)
- (a) Derive a close form solution for the propagation delay high to low, i.e. τ_{PHL} . (20 pts)
 - (b) Solve the integrals for propagation delay high to low and compute the propagation delay τ_{PHL} . Note: $\int \frac{1}{x} dx = \ln(x)$ (20 pts).
 - (c) Derive a close form solution for the propagation delay low to high, i.e. τ_{PLH} . (20 pts)
 - (d) Compute the propagation delay τ_{PLH} . Again note: $\int \frac{1}{x} dx = \ln(x)$ (20 pts).

 

P.3

+ My solution starts.

$$a) \quad i_c = C_{load} \frac{dV_{out}}{dt} = i_{D,p} - i_{D,n}$$

When $H \rightarrow L$, pMos is switched off thus,

$$i_{D,p} = 0.$$

$$C_{load} \frac{dV_{out}}{dt} = -i_{D,n}$$

$$dt = - \frac{C_{load}}{i_{D,n}} dV_{out}$$

$$\int_{t_0}^{t_1} dt = \int_{V_{OH}}^{V_{50\%}} -C_{load} \cdot \frac{1}{i_{D,n}} dV_{out}$$

$$= \int_{V_{OH}}^{V_{50\%}} -C_{load} \cdot R \cdot \frac{1}{V_{out}} dV_{out}$$

$$b) \quad \int_5^{2.5} -C_{load} \cdot R \cdot \frac{1}{V_{out}} dV_{out}$$

$$= -C_{load} \cdot R \cdot \int_5^{2.5} \frac{1}{V_{out}} dV_{out}$$

$$= -1 \cdot 10^{-12} \cdot 10000 \cdot (\ln(2.5) - \ln(5))$$

$$= 6.9314 \cdot 10^{-9}$$

$$= 6.9314 \text{ ns}$$

$$c) \quad i_c = C_{load} \frac{dV_{out}}{dt} = i_{D,p} - i_{D,n}$$

$$dt = \frac{C_{load}}{i_{D,p} - i_{D,n}} dV_{out}$$

$$\int dt = C_{load} \int \frac{1}{i_{D,p} - i_{D,n}} dV_{out}$$

$$= C_{load} \int \left(-\frac{V_{out}}{R} + i_{D,p} \right)^{-1} dV_{out}$$

• Since pMOS is sat.

$$i_{D,p} = \frac{K_n}{2} \left(\frac{W}{L} \right)_n [2(V_{GSn} - V_{Thn}) V_{DSn} - V_{DSn}^2]$$

$$= \frac{10 \cdot 10^{-6}}{2} \cdot \frac{1 \cdot A}{0.9} [2(0 - 1) 5 - 5^2]$$


$$= 10 \cdot 10^{-6} \cdot (-35)$$

$$\int dt = -1 \cdot 10^{-12} \int \left(-\frac{V_{out}}{10000} + 10 \cdot 10^{-6} (-35) \right)^{-1} dV_{out}$$

d)

+ My solution ends.

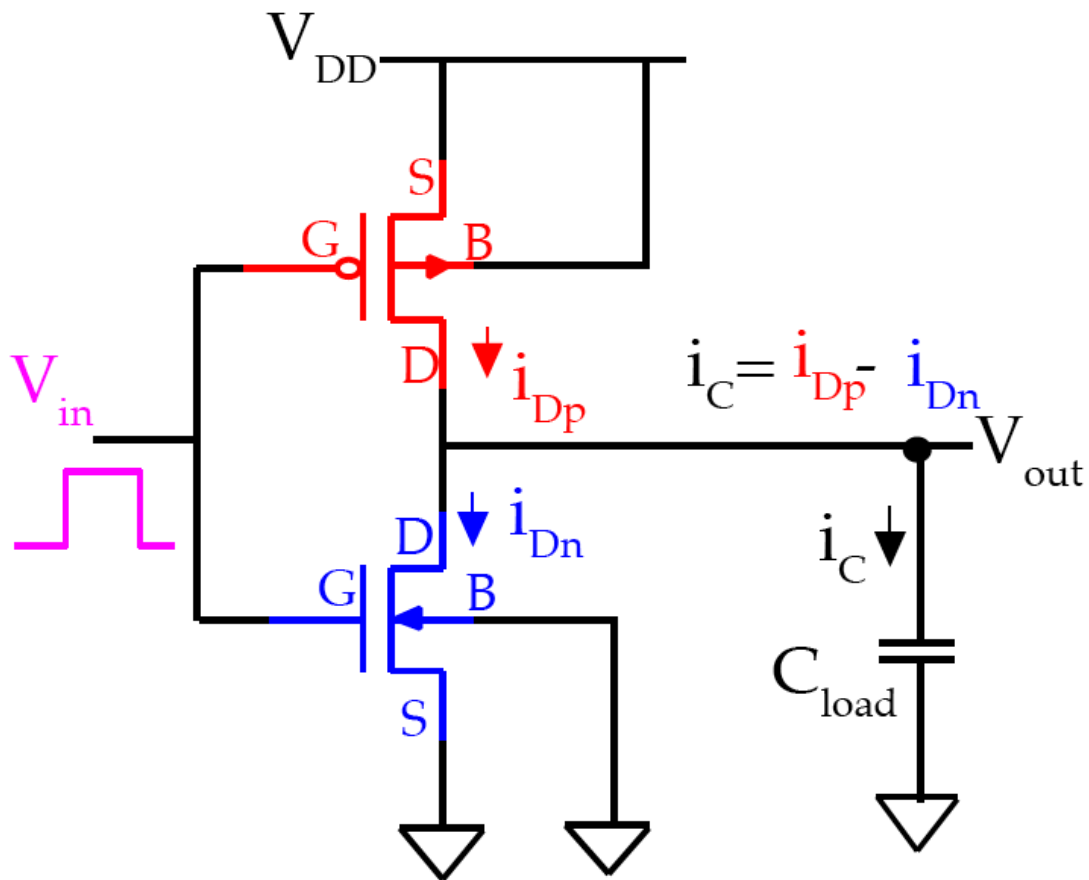P4. Consider the following inverter circuit: (70 pts)



P.4

Transistors parameters are defined as

for nMOS transistor:

$$V_{T0n} = 0.5V; \quad \mu_n C_{ox} = 98 \mu A/V^2; \quad L_n = 40nm;$$

for pMOS transistor:

$$V_{T0p} = -0.48V; \quad \mu_p C_{ox} = 46 \mu A/V^2; \quad L_p = 40nm;$$

This inverter is designed for $V_{TH} = 0.68V$. Also $V_{DD} = 1.2V$

(a) (30pts)

A simplified expression of the total output load capacitance is given as:

$$C_{load} = 5fF + C_{db,n} + C_{db,p}.$$

The drain-substrate parasitic capacitance of the nMOS and pMOS transistors are the functions of the channel width that are defined with a set of simplified capacitance expressions:

$$C_{db,n} = 0.16\text{fF} + (1.7W_n)\text{fF}$$

$$C_{db,p} = 0.13\text{fF} + (1.4W_p)\text{fF}$$

where W_n and W_p are expressed in μm .

Determine the channel width W_n and W_p of both transistors such that the propagation delay HIGH-to-LOW is defined as:

$$\tau_{PHL} \leq 35\text{ps}.$$

+ My solution starts.

$$V_{th} = \frac{V_{T0,n} + \sqrt{\frac{1}{k_R}}(V_{DD} - |V_{T0,p}|)}{1 + \sqrt{\frac{1}{k_R}}}$$

$$0.68 = \frac{0.5 + \sqrt{\frac{1}{k_R}}(1.2 - 0.48)}{1 + \sqrt{\frac{1}{k_R}}}$$

$$k_R = 0.049$$

$$k_R = \frac{k_n}{k_p} = \frac{k'_n(\frac{W}{L})_n}{k'_p(\frac{W}{L})_p} = \frac{98(\frac{W}{L})_n}{46(\frac{W}{L})_p}$$

$$0.049 = \frac{98(\frac{W}{L})_n}{46(\frac{W}{L})_p}$$

$$(\frac{W}{L})_p = 42.953(\frac{W}{L})_n$$

+ Since L_n and L_p is the same, we can get equation below.

$$\boxed{W_p = 43.478W_n}$$

$$\tau_{PHL} = \frac{C_{load}}{k_n(V_{DD} - V_{T0n})} \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PHL} = \frac{C_{load}}{\mu_n C_{ox}(V_{DD} - V_{T0n})} \left(\frac{L_n}{W_n} \right) \left[\frac{2V_{T0n}}{V_{DD} - V_{T0n}} + \ln \left(\frac{4(V_{DD} - V_{T0n})}{V_{DD}} - 1 \right) \right]$$

$$\tau_{PHL} = \frac{C_{load}}{98 \cdot 10^{-6} \cdot (1.2 - 0.5)} \left(\frac{L_n}{W_n} \right) \left[\frac{2 \cdot 0.5}{1.2 - 0.5} + \ln \left(\frac{4(1.2 - 0.5)}{1.2} - 1 \right) \right]$$

$$\tau_{PHL} = \frac{C_{load}}{98 \cdot 10^{-6} \cdot (1.2 - 0.5)} \left(\frac{40 \cdot 10^{-9}}{W_n} \right) \cdot 1.716$$

$$C_{load} = 5fF + 0.16fF + 1.7W_n fF + 0.13fF + 1.4W_p fF$$

$$C_{load} = (5.29 + 1.7W_n + 1.4W_p) fF$$

$$C_{load} = (5.29 + 1.7W_n + 1.4W_p) \cdot 10^{-15}$$

$$\tau_{PHL} = \frac{(5.29 + 1.7W_n + 1.4W_p) \cdot 10^{-15}}{98 \cdot 10^{-6} \cdot (1.2 - 0.5)} \left(\frac{40 \cdot 10^{-9}}{W_n} \right) \cdot 1.716$$

+ Since, $W_p = 43.478W_n$ and $\tau_{PHL} \leq 35ps$.

$$35 \cdot 10^{-12} \geq \frac{(5.29 + 1.7W_n + 1.4 \cdot 43.478W_n) \cdot 10^{-15}}{98 \cdot 10^{-6} \cdot (1.2 - 0.5)} \left(\frac{40 \cdot 10^{-9}}{W_n} \right) \cdot 1.716$$

$$W_n = 1.512 \cdot 10^{-7}$$

$$W_n = 0.1512 \cdot 10^{-6}$$

$$W_n = 0.1512 \mu m$$

+ Since, $W_p = 43.478W_n$

$$W_p = 43.478W_n$$

$$W_p = 43.478 \cdot 0.1512 \mu m$$

$$W_p = 6.573 \mu m$$

$$\boxed{W_p = 6.573 \mu m}$$


$$\boxed{W_n = 0.1512 \mu m}$$

+ My solution ends.

(b) (20pts)

Sketch layout of the inverter from part (a). Include bulk for both transistors. Mark W_n , L_n , W_p and L_p on the sketch of the layout. Specify all regions (n+ active, p+ active, nwell, metal1, metal2, via, contact, and polysilicon). Mark V_{DD} , GND, V_{in} and V_{out} on the sketch of the layout.

+ My solution starts.

 

+ My solution ends.

(c) (20pts)

Assume now that the CMOS inverter shown in figure P.4 has been designed with $(W/L)_n = 10$ and $(W/L)_p = 15$ and that the total output load capacitance is 5fF. Calculate the output rise time τ_{rise} and fall time τ_{fall} using proper equations from the lectures.

+ My solution starts.

$$\tau_{rise} = \frac{C_{load}}{\mu_p C_{ox} \frac{W_p}{L_p} (V_{DD} - |V_{T0p}|)} \left[\frac{2(|V_{T0p}| - 0.1V_{DD})}{V_{DD} - |V_{T0p}|} + \ln \left(\frac{2(V_{DD} - |V_{T0p}|)}{0.1V_{DD}} - 1 \right) \right]$$
$$\tau_{rise} = \frac{5 \cdot 10^{-15}}{46 \cdot 10^{-6} \cdot 15 \cdot (1.2 - 0.48)} \left[\frac{2(0.48 - 0.1 \cdot 1.2)}{1.2 - 0.48} + \ln \left(\frac{2(1.2 - 0.48)}{0.1 \cdot 1.2} - 1 \right) \right]$$

$$\tau_{rise} = 3.419 \cdot 10^{-11}$$

$\tau_{rise} = 34.19 \text{ ps}$

$$\tau_{fall} = \frac{C_{load}}{\mu_n C_{ox} \frac{W_n}{L_n} (V_{DD} - V_{T0n})} \left[\frac{2(V_{T0n} - 0.1V_{DD})}{V_{DD} - V_{T0n}} + \ln \left(\frac{2(V_{DD} - V_{T0n})}{0.1V_{DD}} - 1 \right) \right]$$
$$\tau_{fall} = \frac{5 \cdot 10^{-15}}{98 \cdot 10^{-6} \cdot 10 \cdot (1.2 - 0.5)} \left[\frac{2(0.5 - 0.1 \cdot 1.2)}{1.2 - 0.5} + \ln \left(\frac{2(1.2 - 0.5)}{0.1 \cdot 1.2} - 1 \right) \right]$$

$$\tau_{fall} = 2.516 \cdot 10^{-11}$$

$\tau_{fall} = 25.16 \text{ ps}$

+ My solution ends.