McKelvey School of Engineering

Spring Semester 2023

CSE463M: Digital Integrated Circuit Design and Architecture
Final Assign #2 - Schematic

Sterling Lech
Byeongchan Gwak

- * There are many parts to complete the Simplified DES.
- * Below is the list of all parts.

For basic operation

INVERTOR

NAND

XOR

XOR4

For bit control

P10

P8

P4

SHIFT 1

SHIFT 3

EP

SWITCH

IΡ

IP Invert

For selection

2:1 mux

16:1 mux

For Enable

ENABLE

For CLK

D-LATCH


D Flip flop

For SBox


SBox Red

SBox Green


* INVERTOR

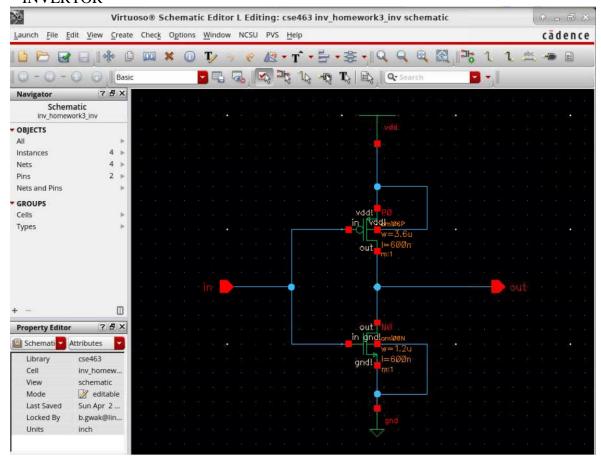


* NAND

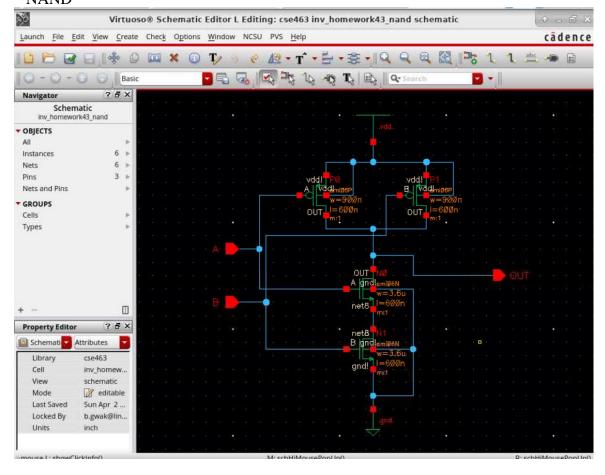


* XOR

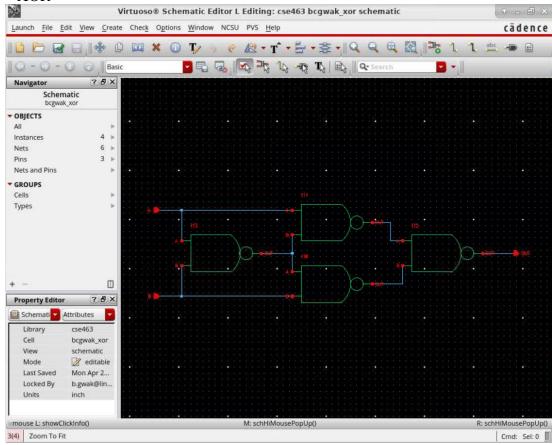



* XOR4

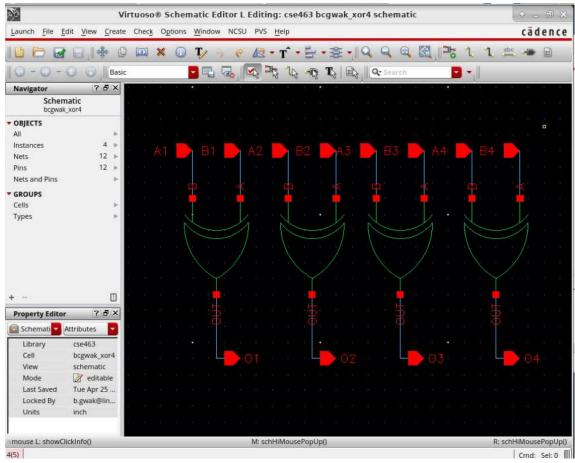

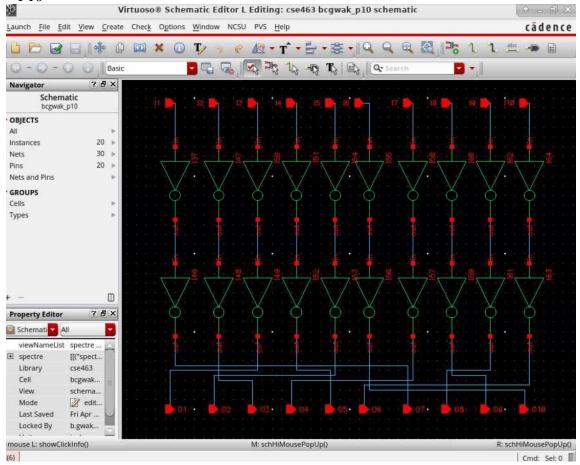


* P8

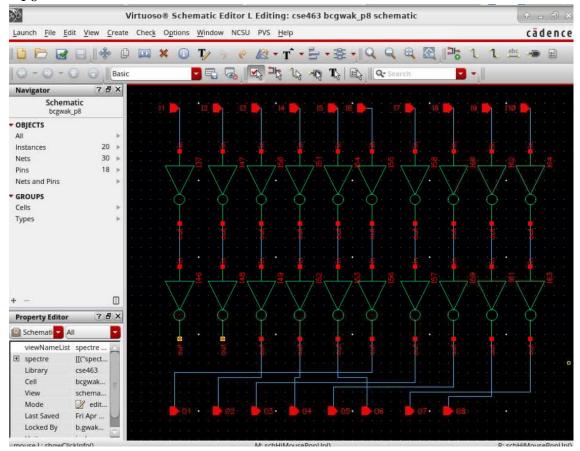


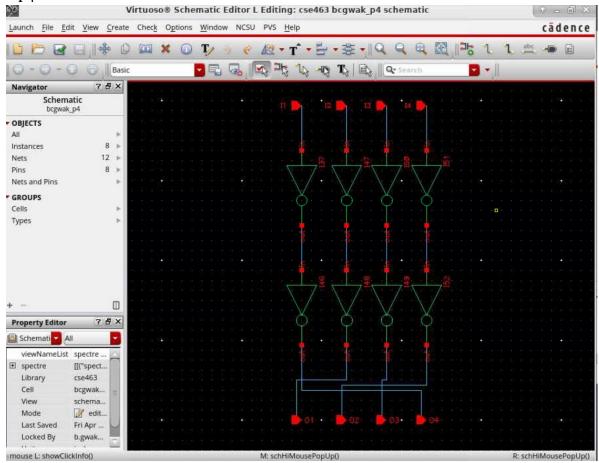


* SHIFT 1

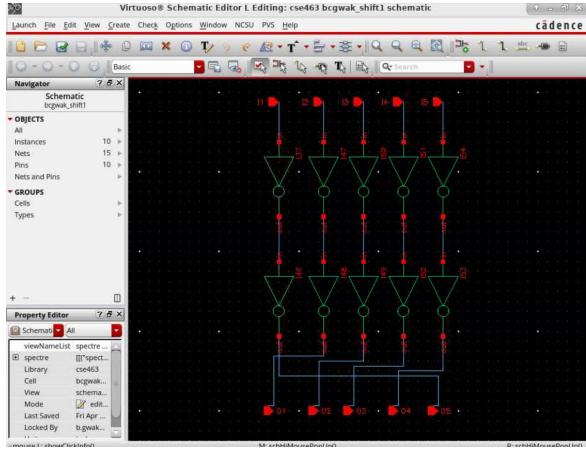


* SHIFT 3

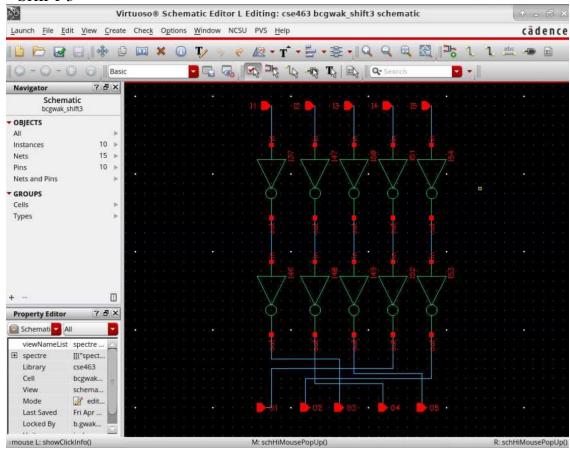


* EP

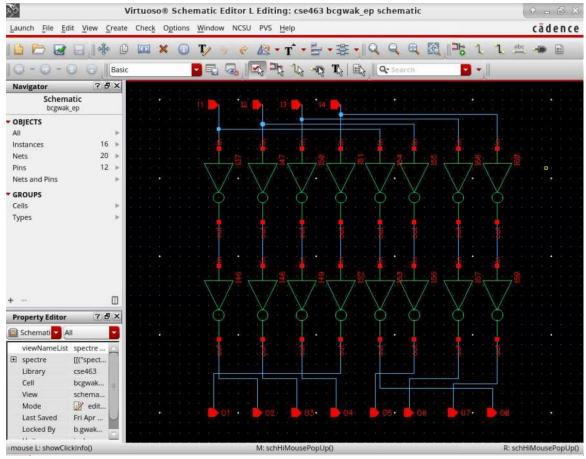


* SWITCH

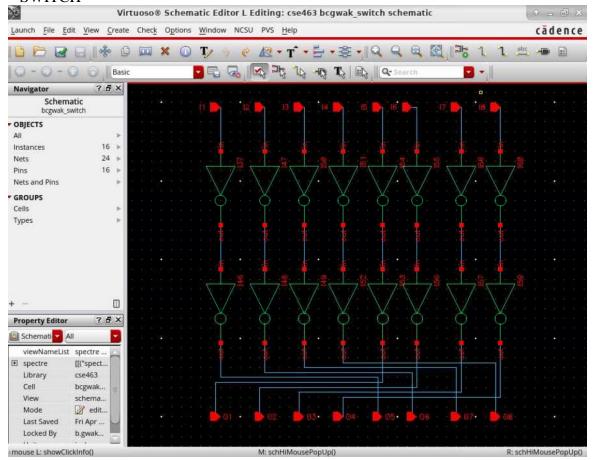


* IP

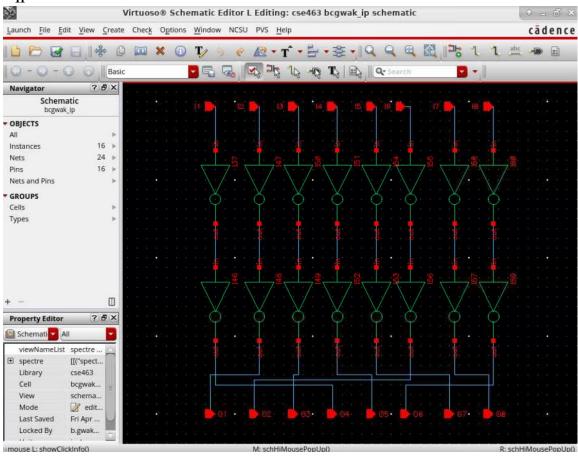


* IP Invert

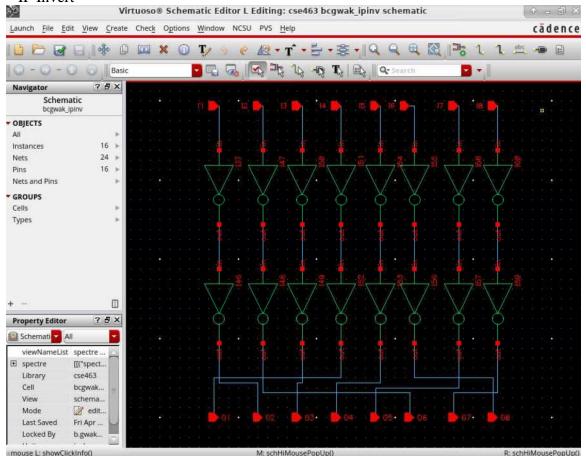


* 2:1 mux

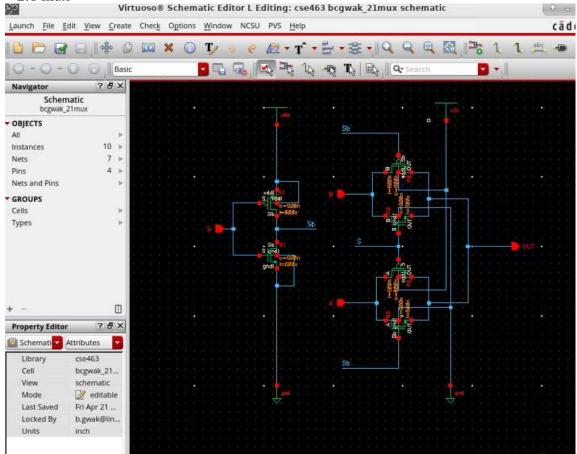


* ENABLE

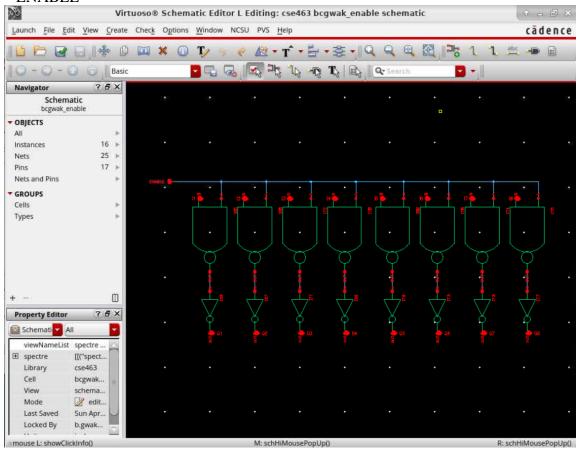


* D-LATCH

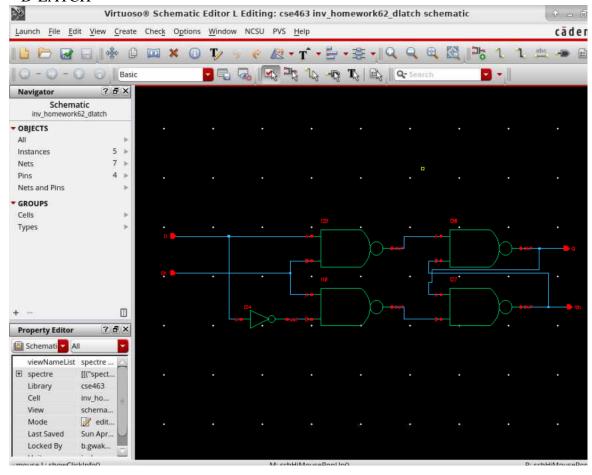




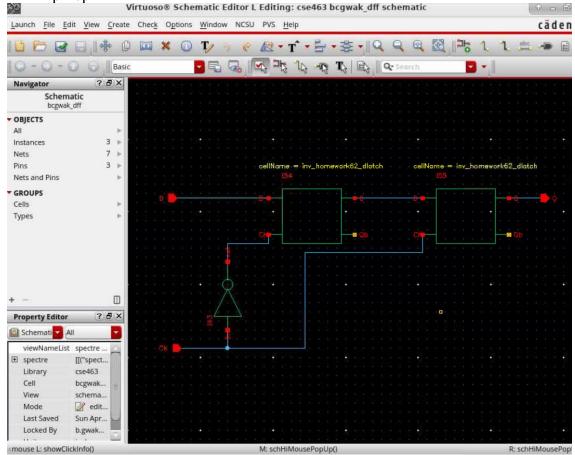



* SBox Red

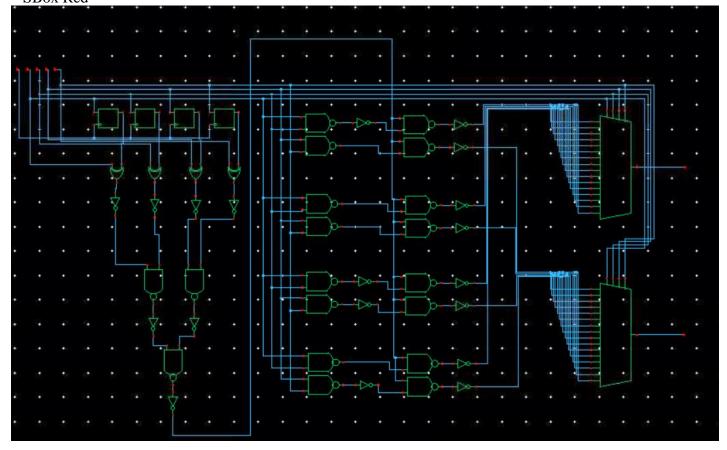

* SBox Green

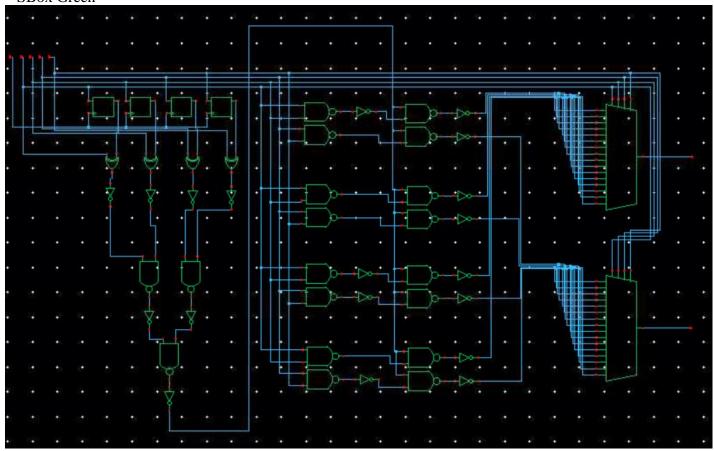

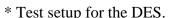

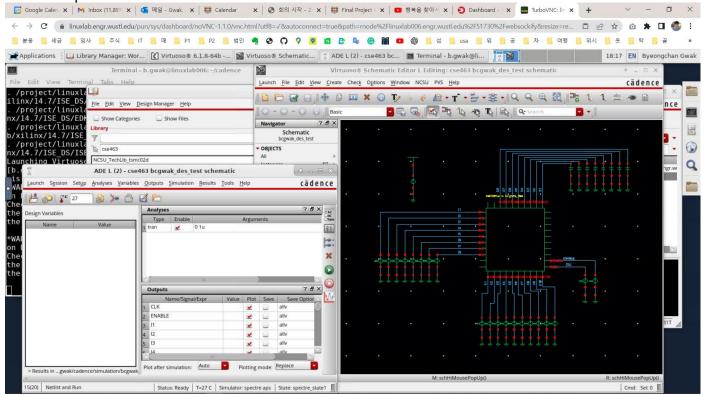

* Whole DES schematic. It's a bit long and I split the image file in half. Below is the first one.

* Below is the second half. 1 02 03 04 05 06 07 08

